

Lab. 04

Logic Design Lab.

Spring 2022

Prof. ChangGun Lee

(cglee@snu.ac.kr)

TA. Hayeon Park

TA. Seohwan Yoo

TA. Haejoo Jeon


(ta@rubis.snu.ac.kr)

Contents

- **BCD to 7-segment Decoder**
- **Lab**
- **Homework**


BCD to 7-segment Decoder

7-segment Display

 


- A form of electronic display device for displaying decimal numerals that is an alternative to the more complex dot-matrix displays.
- Widely used in digital clocks, electronic meters, and other electronic devices for displaying numerical information.

BCD to 7-segment Decoder

 

We need a decoder like above
So we will make it

BCD to 7-segment Decoder (cont'd)

 

Step

1. Make a truth table with BCD and 7-segment outputs
2. Make Boolean expressions according to the table
3. Minimize them
4. Implement a decoder according to the expressions

Lab

Today


- **Implement BCD to 7-segment Decoder** on Xilinx ISE in
 - 1) Structural description
 - 2) Data-flow style description
 - 3) Behavioral descriptionand simulate each of them

Homework

- **Implement 'Klingon number system' Decoder for 7-segment on Xilinx ISE in**

- 1) Structural description
- 2) Data-flow style description
- 3) Behavioral description

and simulate each of them

 

Pic. Klingon number system

Report

- **Lab part**

1. Xilinx source code
2. Result of simulation

- **Homework part**

1. Truth table, Karnaugh map, Boolean expression
2. Xilinx source code
3. Result of simulation


- **Due**

- 4 / 18 (Mon) Class 001
- 4 / 19 (Tue) Class 002
- 4 / 20 (Wed) Class 003




Report

- We can't see your picture.
 - Please **don't capture the whole screen** but only the proper bound of the screen.
 - Also don't take picture of your monitor. Capture the page.
 
```
21 module v74x139(  
22     input G1,  
23     input G2,  
24     input A1,  
25     input A2,  
26     input B1,  
27     input B2,  
28     output [3:0] Y1,  
29     output [3:0] Y2  
30 );  
31  
32     v74x139h T1(.G(G1), .A(A1), .B(B1), .Y(Y1));  
33     v74x139h T2(.G(G2), .A(A2), .B(B2), .Y(Y2));  
34  
35 endmodule  
36
```



Good case

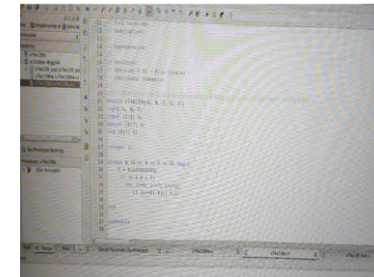  

Bad case

Questions
