

# Lab. 07

Logic Design Lab.

Spring 2022

Prof. ChangGun Lee

([cglee@snu.ac.kr](mailto:cglee@snu.ac.kr))

TA. Hayeon Park

TA. Haejoo Jeon

TA. Seohwan Yoo

([rubis.ld.ta@gmail.com](mailto:rubis.ld.ta@gmail.com))

# Contents

---






- **Synchronous Binary Counter**
- **Frequency Divider**
- **Implementation on Logic Design Board (Review)**
- **Two Digit Counter**

# Announcement


---

- There will be an announcement of the final project in next lab session.
- Please make sure your board is working correctly

# Filp Flops (Recap)

     
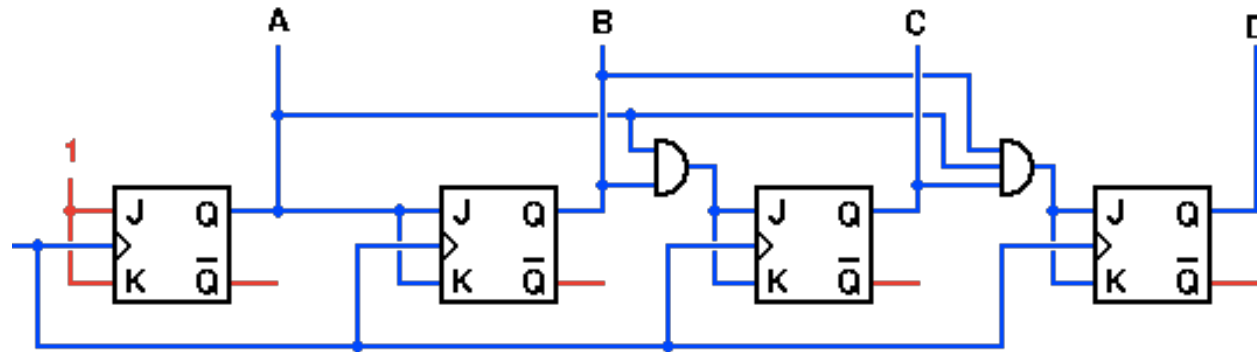
# 4-bit Counter – JK Flip Flop Implementation




- J-K flip-flop functions as a T flip-flop if you connect the same input to J and K.
- A will repeat 0 and 1.

JK	J	K	Q(next)
	0	0	Q
	0	1	0
	1	0	1
	1	1	Q'

T	T	Q(next)
	0	Q
	1	Q'

States				Count
D	C	B	A	
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9
1	0	1	0	10
1	0	1	1	11
1	1	0	0	12
1	1	0	1	13
1	1	1	0	14
1	1	1	1	15
 
# Frequency Divider – JK Flip Flop Implementation



JK


J	K	$Q(\text{next})$
0	0	Q
0	1	0
1	0	1
1	1	$Q'$

negative edge triggered JK Flip Flop

# Implementation on Logic Design Board (Review)

---

# SNU Logic Design Board

 

- ① Power Input : Molex Connector (DC 5V Only)
- ② Power , DONE LED
- ③ FPGA : XC3S50AN-4TQG144C
- ④ User I/O Ports (P1) : 16X2 2.54mm Pitch
- ⑤ User I/O Ports (P2) : 16X2 2.54mm Pitch
- ⑥ User I/O Ports (P3, P4) : 2 8X2 2.54mm Pitch
- ⑦ User Output LEDs : 6 output LEDs
- ⑧ User Output LEDs : 6 7-segment LEDs
- ⑨ User Input Switches : 10pin Dip Switch
- ⑩ User Input Switches : 6 Tactile Switches
- ⑪ Oscillator : 50MHz
- ⑫ Mode Select Switch
- ⑬ JTAG Header



# SNU Logic Design Board

- Pin Number Mapping

Pin Num	Component	
P1	3	A
	4	B
	5	C
	6	D
	7	E
	8	F
	10	G
	11	A
	12	B
	13	C
	15	D
	16	E
	18	F
	19	G
	20	A
	21	B
	24	C
	25	D
	27	E
	28	F
	29	G
	30	1
	31	2
	32	3
	33	4
	41	5
	42	6
	43	7
	44	8
	45	9
	46	10
	47	Tactile Switch [SW1]

Pin Num	Component	
P2	48	Tactile Switch [SW2]
	49	Tactile Switch [SW3]
	50	Tactile Switch [SW4]
	51	Tactile Switch [SW5]
	54	Tactile Switch [SW6]
	55	A
	58	B
	59	C
	60	D
	62	E
	63	F
	64	G
	68	A
	69	B
	70	C
	71	D
	72	E
	75	F
	76	G
	77	A
	78	B
	79	C
	82	D
	83	E
	84	F
	85	G
	87	LED [D1] Red
	88	LED [D2] Yellow
	90	LED [D3] Green
	91	LED [D4] Red
	92	LED [D5] Yellow
	93	LED [D6] Green

Pin Num	Component	
P3	96	
	98	
	99	
	101	
	102	
	103	
	104	
	105	
	110	
	111	
	112	
	113	
	114	
	115	
	116	
	117	



Pin Num	Component	
P4	120	
	121	
	124	
	125	
	126	
	127	
	129	
	130	
	131	
	132	
	134	
	135	
	138	
	139	
	141	
	142	

Pin	Component	
FPGA	57	Clock 50MHz
	14	
	23	
	40	
	61	VCCO
	86	
	95	
	119	
	136	
	36	VCCAUX
	66	
	108	
	133	
	22	VCCINT
	52	
	94	
	122	
	9	
	17	
	26	
	34	
	56	
	65	
	81	GND
	89	
	100	
	106	
	118	
	128	
	137	

Pin	Component	
JP101	1	TMS
	2	TDI
	107	TDO
	109	TCK
Mode SW	37	M1
	38	M0
	39	M2
	144	PROG
FPGA	67	INIT
	73	DONE
	74	SUSPEND
	35	
FPGA	53	Not Connected (Input Only/VREF)
	80	
	97	
	123	
	140	



# SNU Logic Design Board

- Assign I/O pins for the half adder

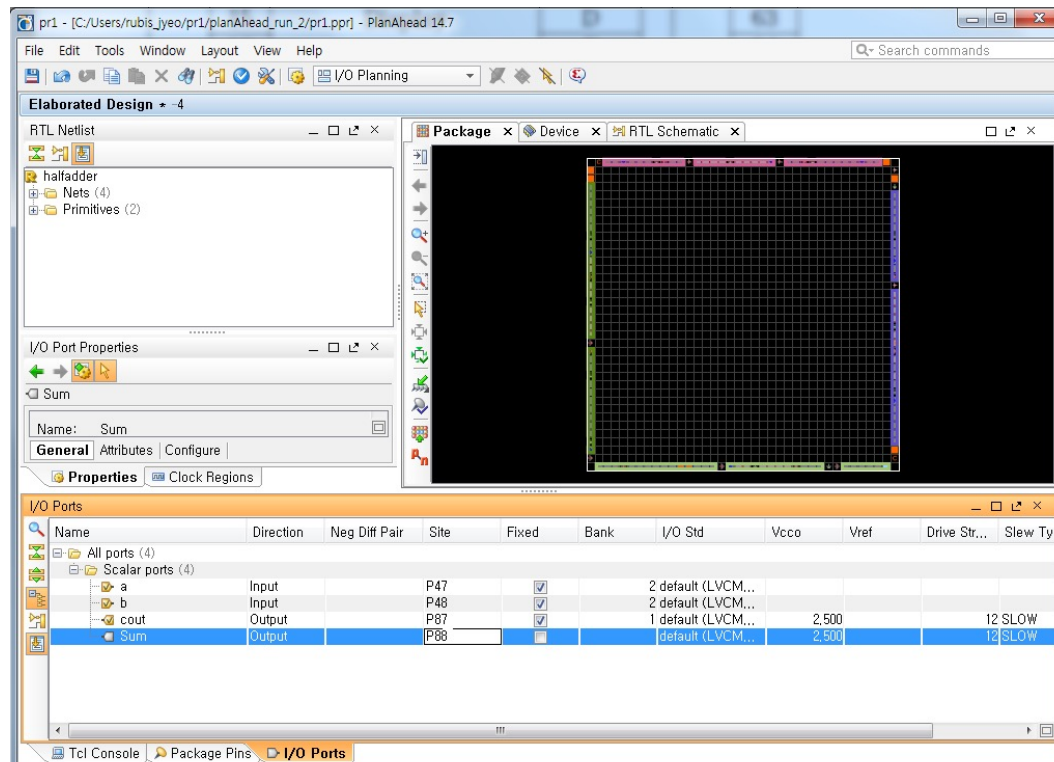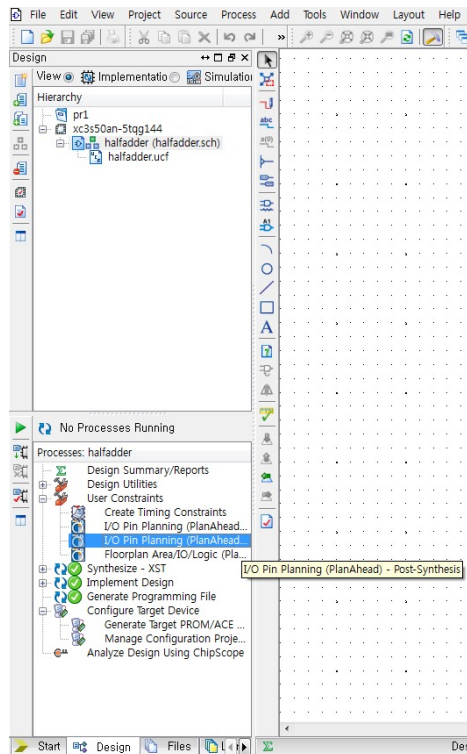


# SNU Logic Design Board

- Boundary Scan > Initialize Chain

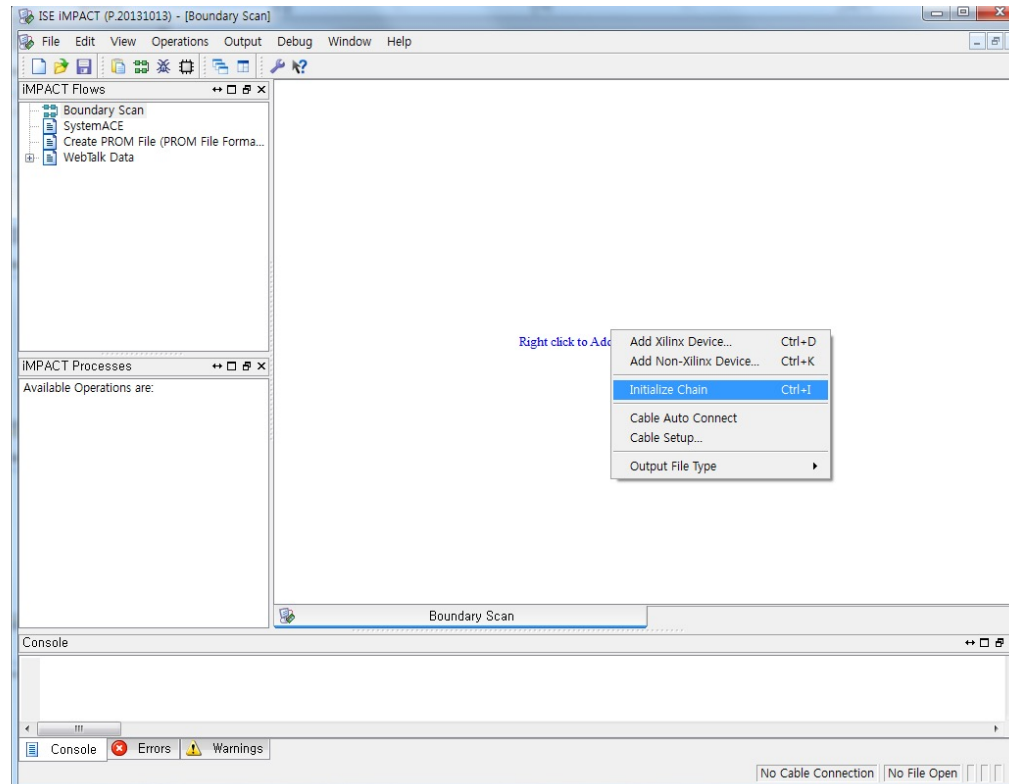 

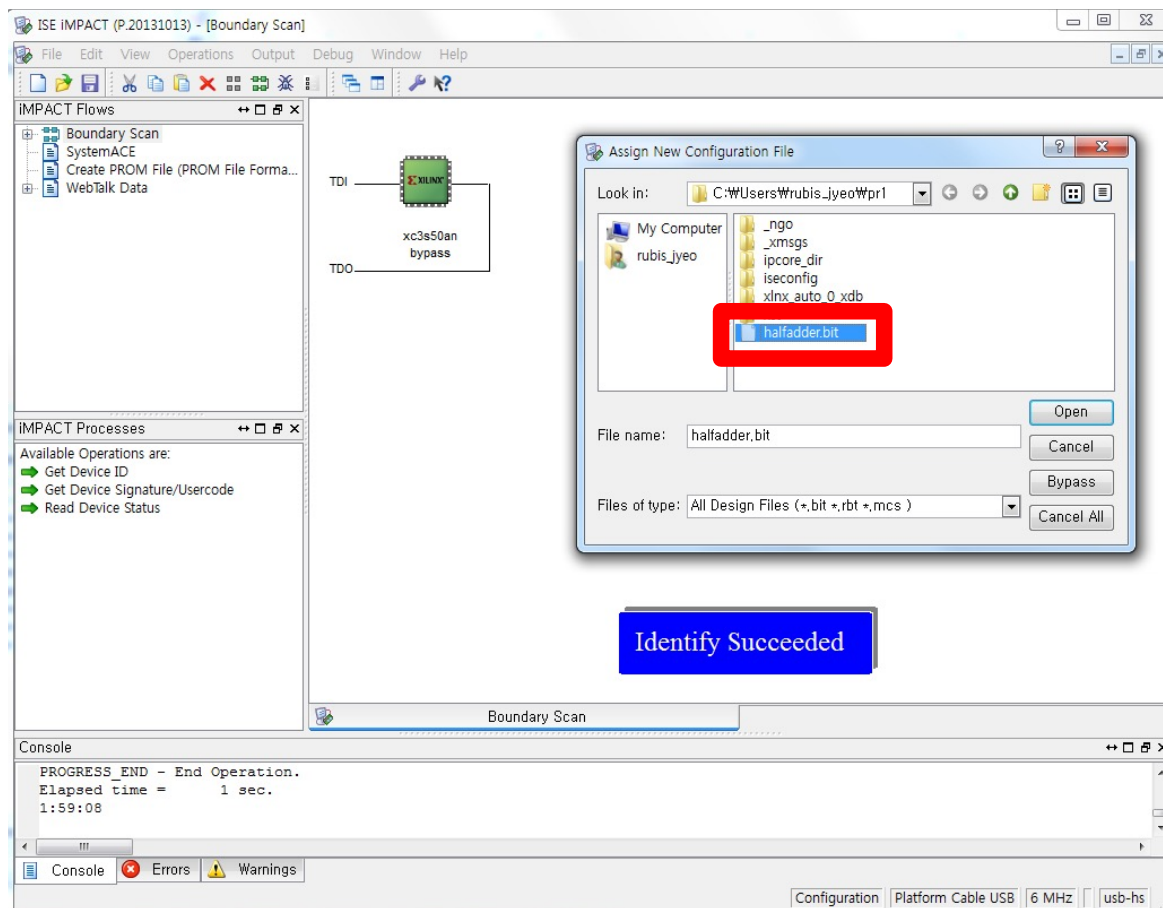
# SNU Logic Design Board

- Choose the schematic source you've written.



# SNU Logic Design Board


- Program FPGA Only > Program Succeeded

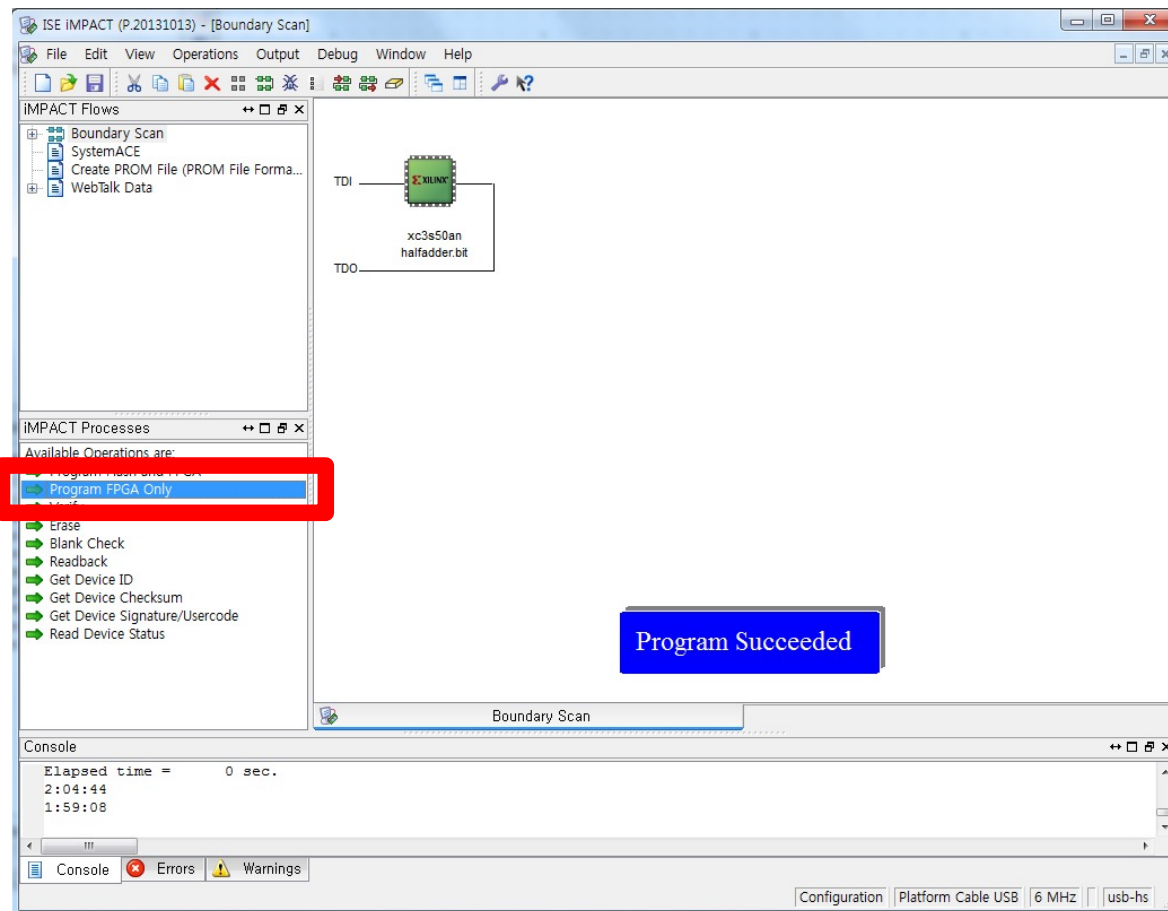

# Two Digit Counter

---

# Two Digit Counter Structure

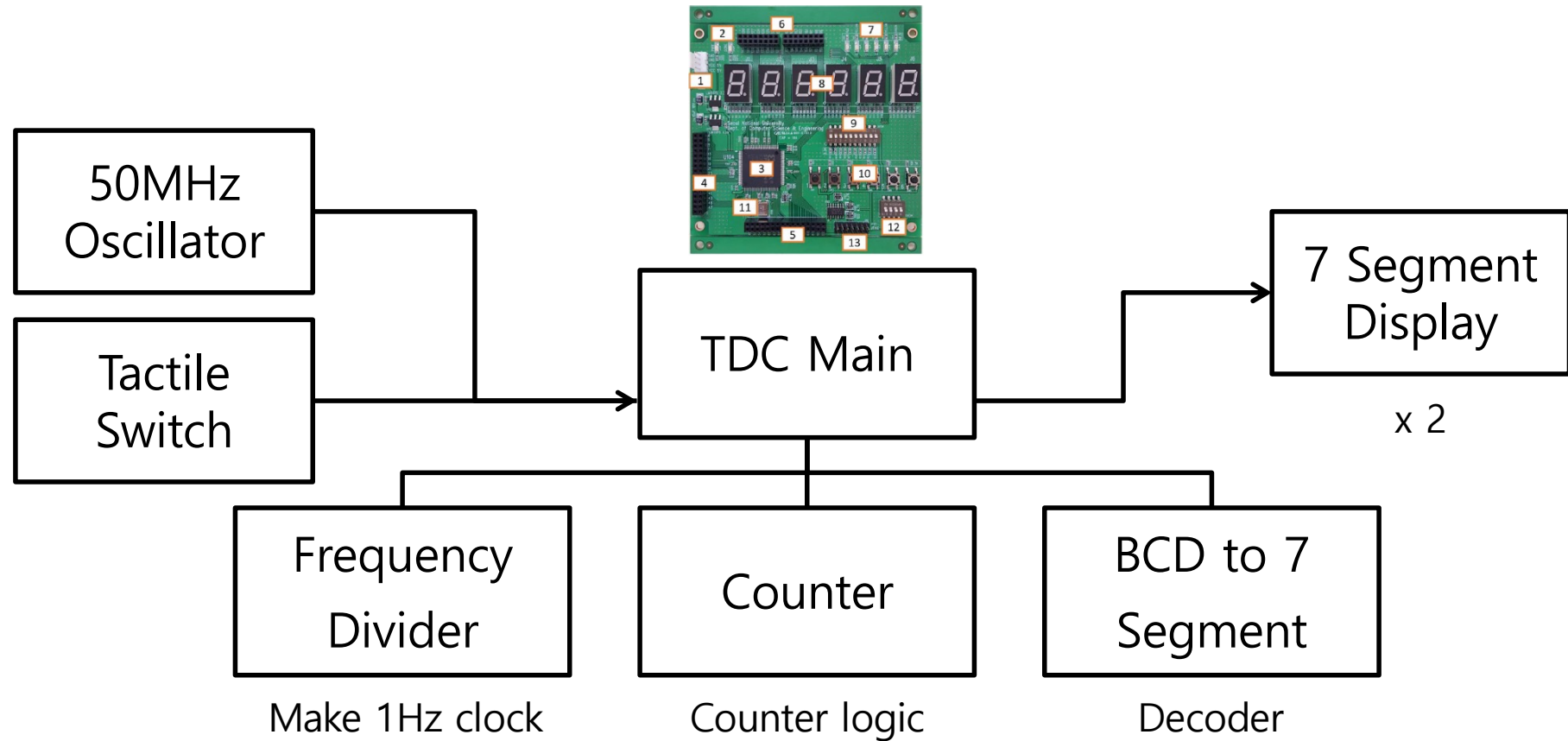

# Homework

---

1. Implement the **Counter** Module in Verilog. It should start from 0, and increment 1 every **positive edge of clock**. The next value of 99 should be 0. Additionally, your implementation should handle external reset signal, it should set the counter back to 0 when the signal is HIGH.



# Homework

---

2. Implement the **Two Digit Counter** in Verilog and upload your implementation to the Logic Design Board. It should start from 0, and increment 1 **every second**. The next value of 99 should be 0. Additionally, your implementation should handle external reset signal, it should set the counter back to 0 when the signal is HIGH. Use 50MHz oscillator (pin 57) as clock input, and a tactile switch (pin 47) as reset button. Also, use two 7-segment displays as your two-digit output.

# Sample Code (Behavioral Description)

```
`timescale 1ns / 1ps

module freq_divider(
    input clr,
    input clk,
    output reg clkout
);
    reg[31:0] cnt;
    always@ (posedge clk) begin
        if(clr) begin
            cnt <= 32'd0;
            clkout <= 1'b0;
        end
        else if (cnt == 32'd25000000) begin
            cnt <= 32'd0;
            clkout <= ~clkout;
        end
        else begin
            cnt <= cnt + 1;
        end
    end
end
endmodule
```

Frequency Divider

```
1 `timescale 1ns / 1ps
2
3 module bcd_to_7(
4     input [3:0] bcd,
5     output reg [6:0] seg
6 );
7
8     always@(bcd) begin
9         case(bcd)
10             4'd0: seg <= 7'b0111111;
11             4'd1: seg <= 7'b0000110;
12             4'd2: seg <= 7'b1011011;
13             4'd3: seg <= 7'b1001111;
14             4'd4: seg <= 7'b1100110;
15             4'd5: seg <= 7'b1101101;
16             4'd6: seg <= 7'b1111101;
17             4'd7: seg <= 7'b0000111;
18             4'd8: seg <= 7'b1111111;
19             4'd9: seg <= 7'b1101111;
20         endcase
21     end
22
23 endmodule
```

BCD to 7-segment Decoder

# Homework

- **Hint : There is modular operation in Verilog. But..**
  - Our board does not support division by 10.
  - We recommend using 4 bit for each digit in counter logic


```
wire [6:0] bcd;  
wire [3:0] ten_bcd;  
wire [3:0] one_bcd;  
  
assign ten_bcd = bcd / 10;  
assign one_bcd = bcd % 10;
```

```
Console  
===== *  
HDL Analysis *  
=====  
Analyzing top module <tdc_main>.  
✖ ERROR:Xst:867 - "tdc_main.v" line 15: Operator / is only supported when the second operand is a power of 2.  
✖ ERROR:Xst:867 - "tdc_main.v" line 16: Operator % is only supported when the second operand is a power of 2.  
  
Found 2 error(s). Aborting synthesis.  
-->
```
 
# Homework

- **Simulating 50MHz clock in test bench**

- 50MHz : period is 20ns  
(So we should flip clock every 10ns)



```
`timescale 1ns / 1ps

module counter_sim;

    // Inputs
    reg clk;
    reg reset;

    // Outputs
    wire [6:0] cnt;

    // Instantiate the Unit Under Test (UUT)
    counter uut (
        .clk(clk),
        .reset(reset),
        .cnt(cnt)
    );

    always #10 clk=~clk;


    initial begin
        // Initialize Inputs
        clk = 0;
        reset = 1;
    end

endmodule
```

# Homework

---

- Remind) Simulating more than 1ms

 



# Report

## ▪ Counter Module (Verilog)
  
### 1. Result of simulation (should attach waveform of three case)

- should increase 1 in normal case
- should set 0 when counter = 100
- should be 0 when reset = 1

(The bus value of the counter must be **clearly visible** in picture)



## ▪ Two Digit Counter

### 1. All Verilog source code

- should include code for module, submodule (i.e., TDC main, counter, freq divider, BCD-7 seg decoder)
- only module code, **no test bench code**

### 2. Result of implementation of three case

- should increase 1 in normal case
- should set 0 at t = 100s
- should be 0 when pressing the reset button (at least 2 pictures should be attached for each case)

## ▪ Discussion

# Report

---

- Write a report
  - Either in Korean or in English
  - **Your report should include**
    - Discussion
    - Homework
  - # of pages doesn't matter
  - Documents should be submitted as PDF file(**less than 25Mb**)
  - **Attach source code and waveform screenshot**
  - Due :
    - Class 001 - May, 9<sup>th</sup> (Before class begin at 7:00pm)
    - Class 002 - May, 10<sup>th</sup> (Before class begin at 7:00pm)
    - Class 003 - May, 11<sup>th</sup> (Before class begin at 7:00pm)