

Lab. 08

Logic Design Lab.

Spring 2022

Prof. ChangGun Lee

(cglee@snu.ac.kr)

TA. Hayeon Park

TA. Haejoo Jeon

TA. Seohwan Yoo

(rubis.ld.ta@gmail.com)


Contents

- **Finite state machine**
- **Moore/Mealy machine**
- **Implementation on Logic Design Board**
- **Vending machine**

Announcement


- There will be an announcement of the final project in next lab session.
- Please make sure your board is working correctly

Finite state machine

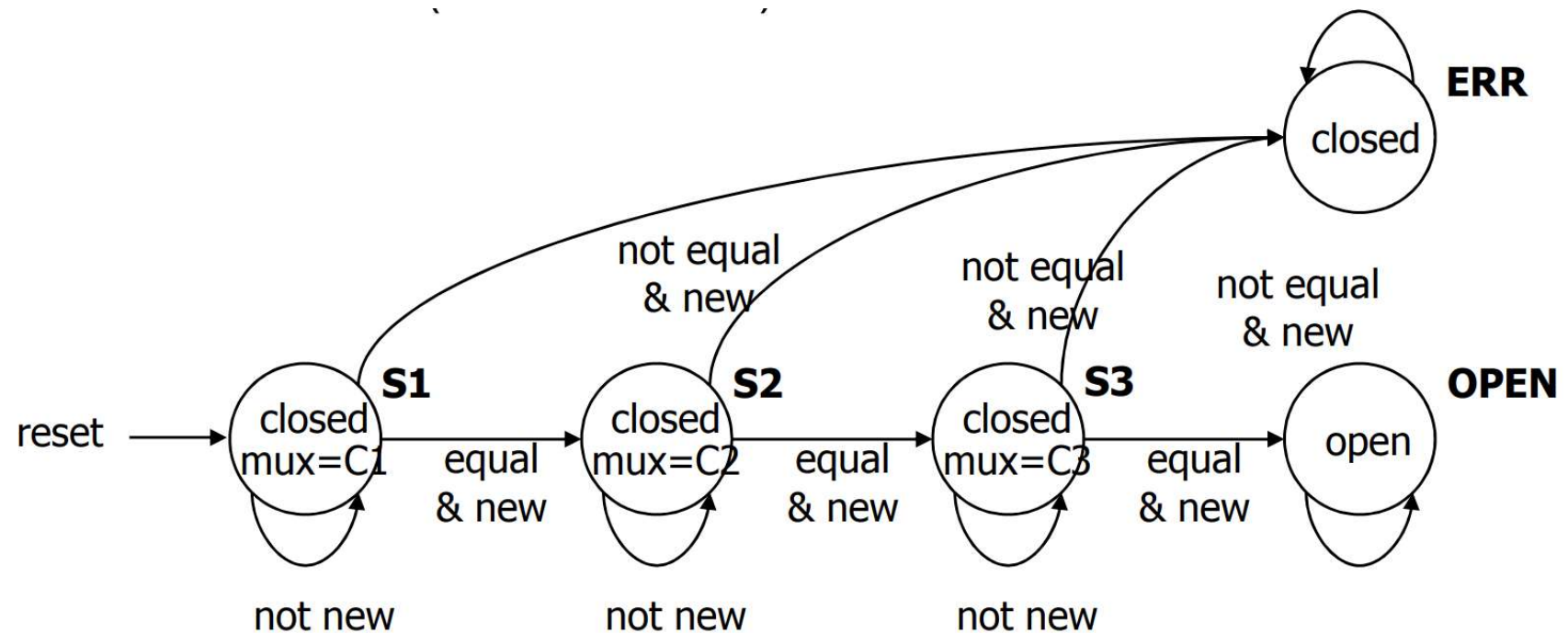


Moore/Mealy machine

- MOORE

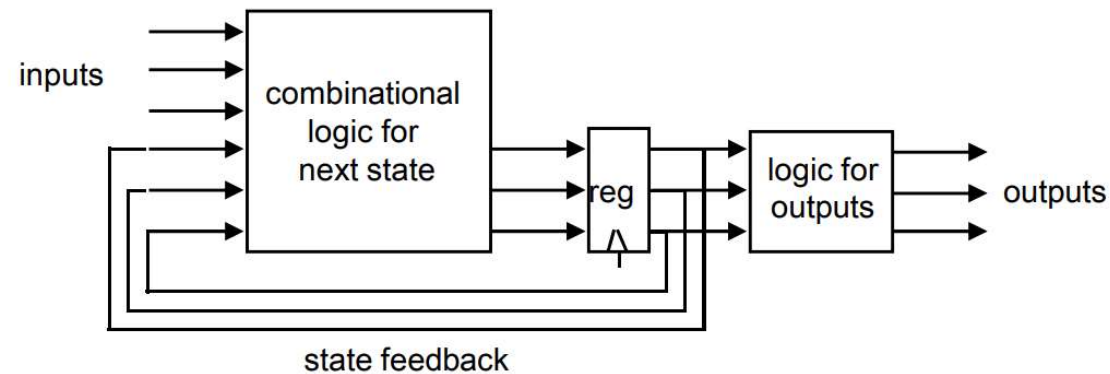


- MEALY

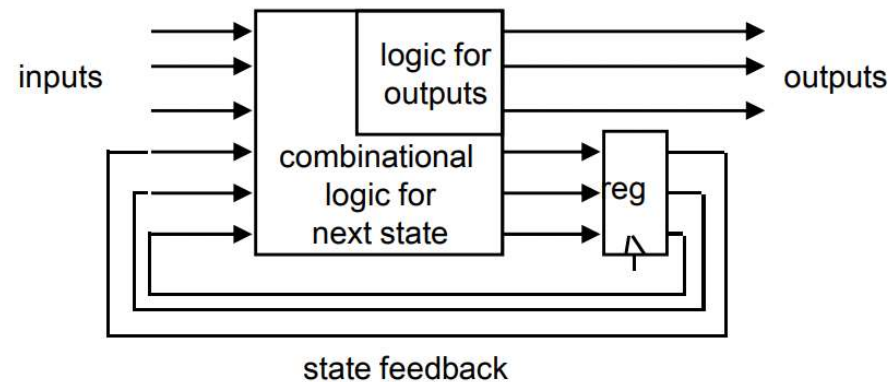

Implementation on Logic Design Board (Review)

SNU Logic Design Board

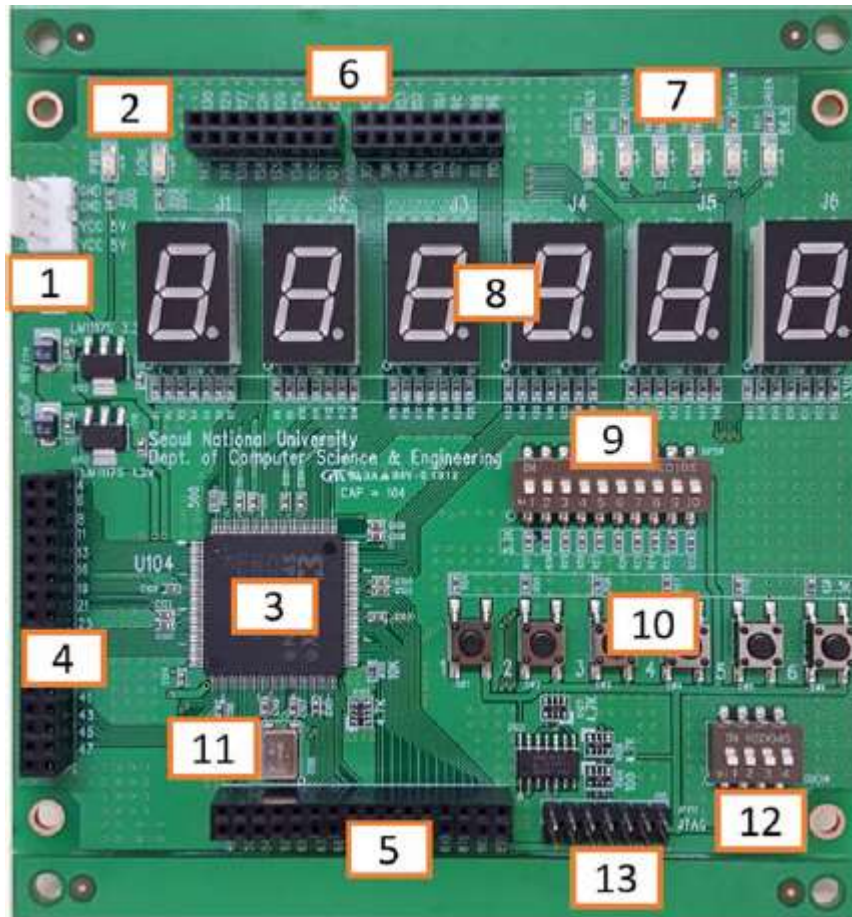

- ① Power Input : Molex Connector (DC 5V Only)
- ② Power, DONE LED
- ③ FPGA : XC3S50AN-4TQG144C
- ④ User I/O Ports (P1) : 16X2 2.54mm Pitch
- ⑤ User I/O Ports (P2) : 16X2 2.54mm Pitch
- ⑥ User I/O Ports (P3, P4) : 2 8X2 2.54mm Pitch
- ⑦ User Output LEDs : 6 output LEDs
- ⑧ User Output LEDs : 6 7-segment LEDs
- ⑨ User Input Switches : 10pin Dip Switch
- ⑩ User Input Switches : 6 Tactile Switches
- ⑪ Oscillator : 50MHz
- ⑫ Mode Select Switch
- ⑬ JTAG Header



SNU Logic Design Board

- Pin Number Mapping

Pin Num	Component
P1	3
	4
	5
	6
	7
	8
	10
	11
	12
	13
	15
	16
	18
	19
	20
	21
	24
	25
	27
	28
	29
	30
	31
	32
	33
	41
	42
	43
	44
	45
	46
	47
	48
	49
	50
	51
	54
	55
	58
	59
	60
	62
	63
	64
	68
	69
	70
	71
	72
	75
	76
	77
	78
	79
	82
	83
	84
	85
	87
	88
	90
	91
	92
	93
	96
	98
	99
	101
	102
	103
	104
	105
	110
	111
	112
	113
	114
	115
	116
	117
	120
	121
	124
	125
	126
	127
	129
	130
	131
	132
	134
	135
	138
	139
	141
	142
	143
	730



SNU Logic Design Board

- Assign I/O pins for the half adder

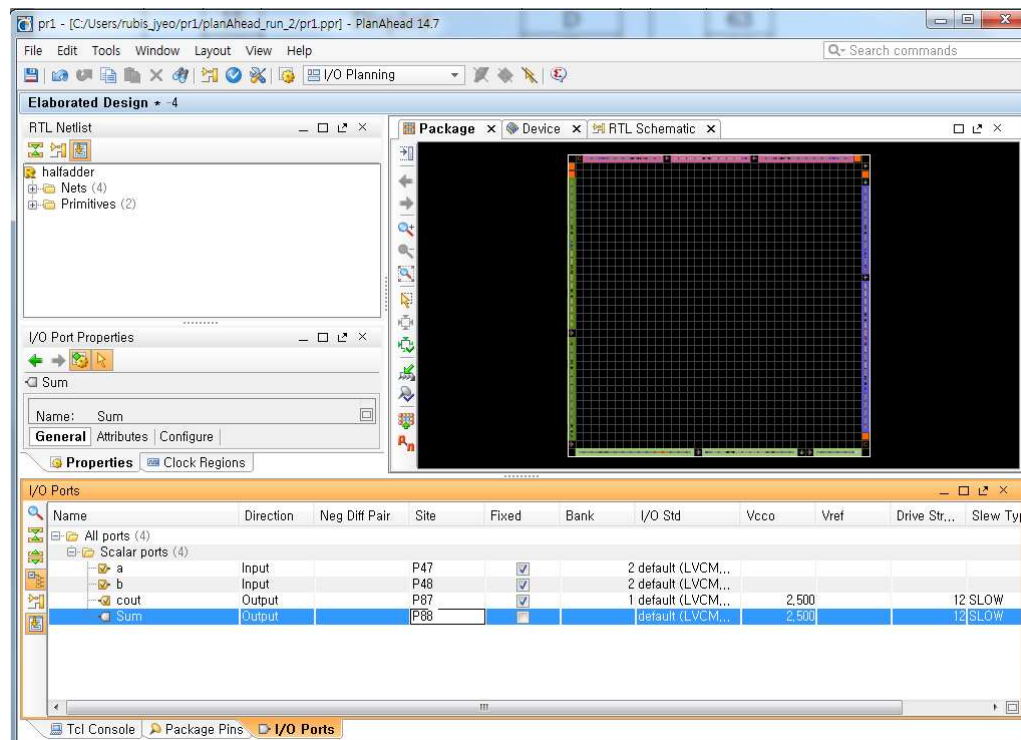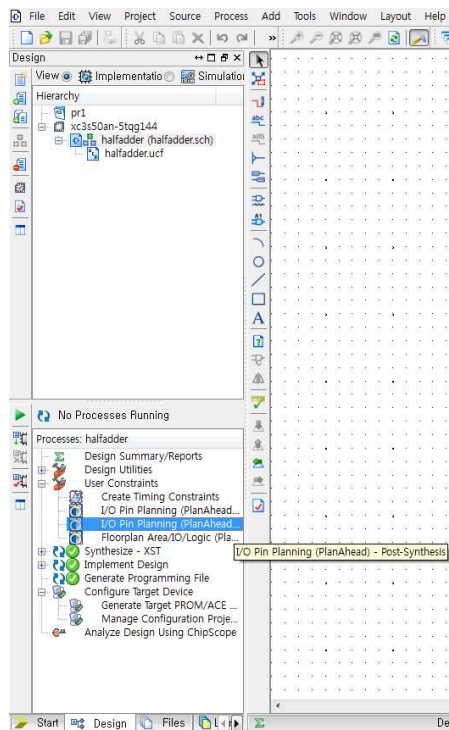


SNU Logic Design Board

- Boundary Scan > Initialize Chain

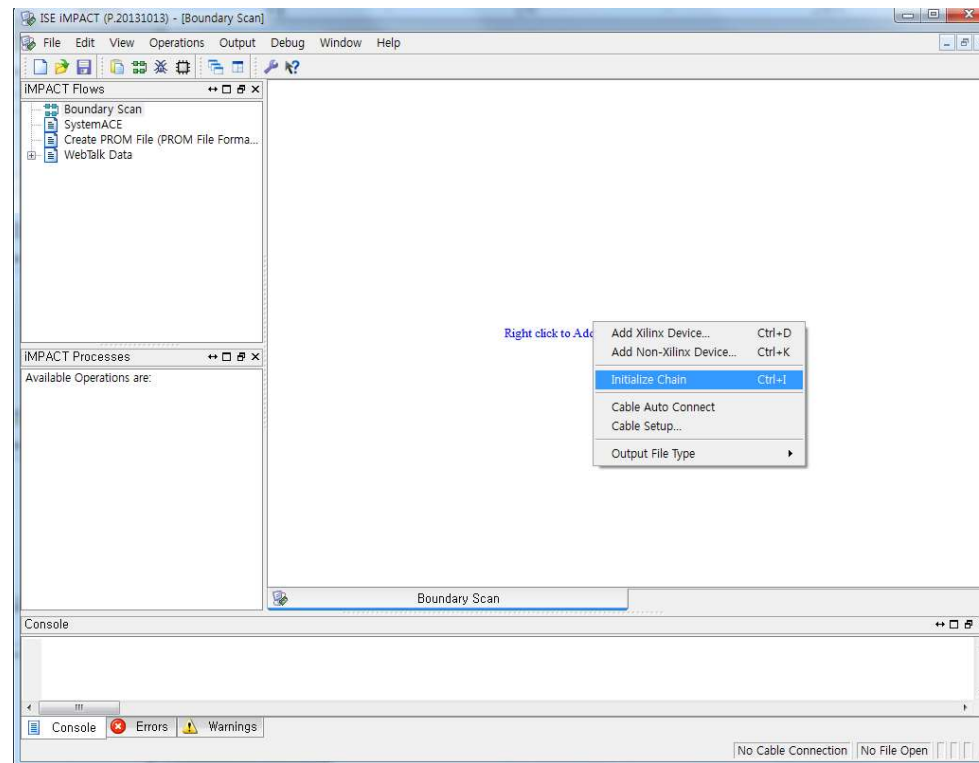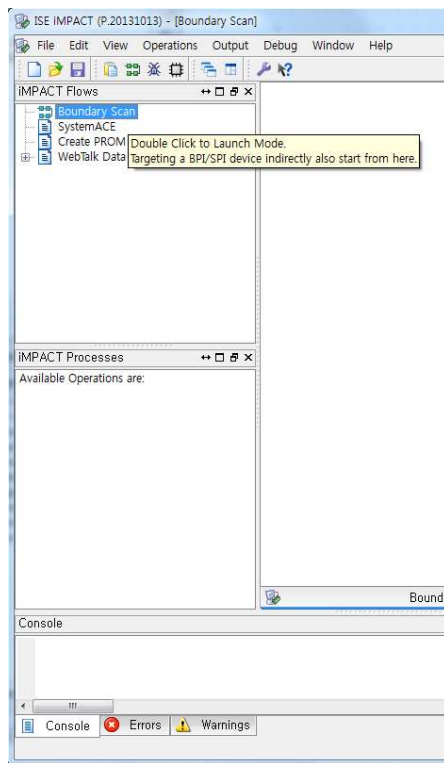


SNU Logic Design Board

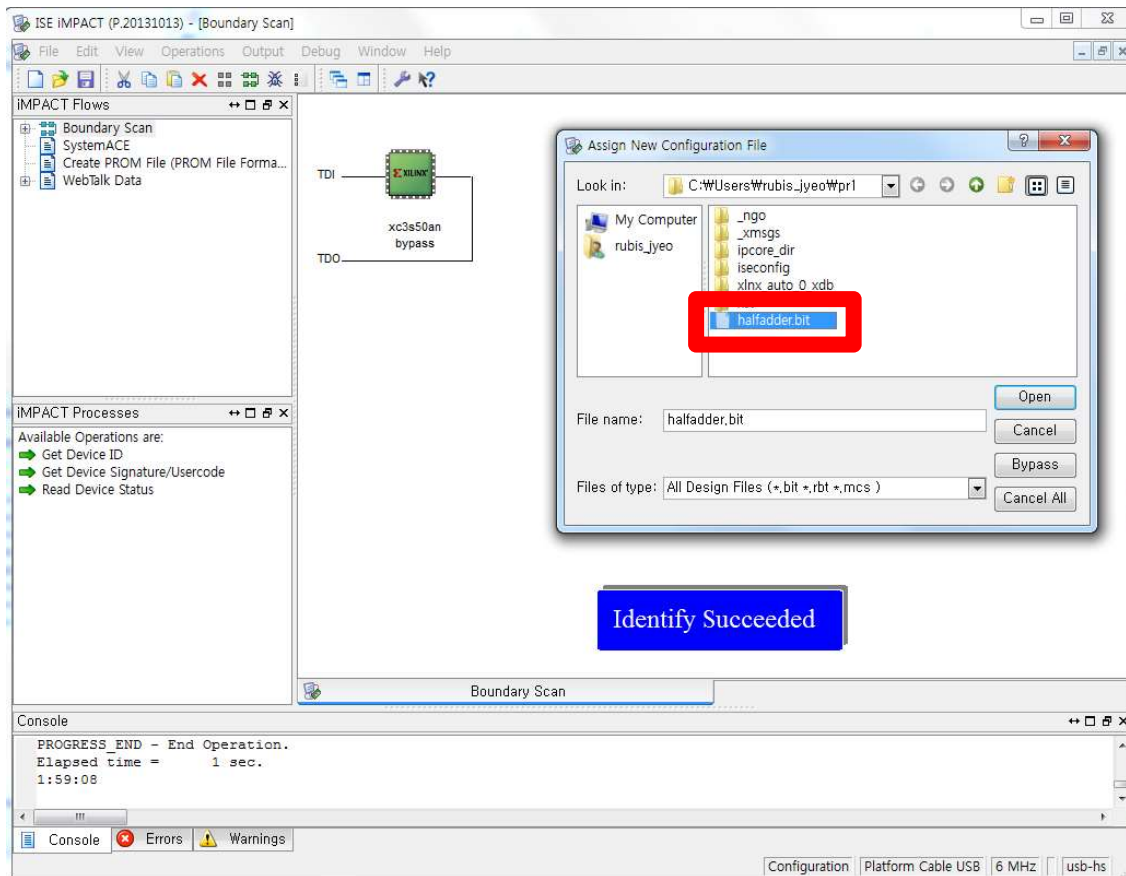- Choose the schematic source you've written.




SNU Logic Design Board

- Program FPGA Only > Program Succeeded

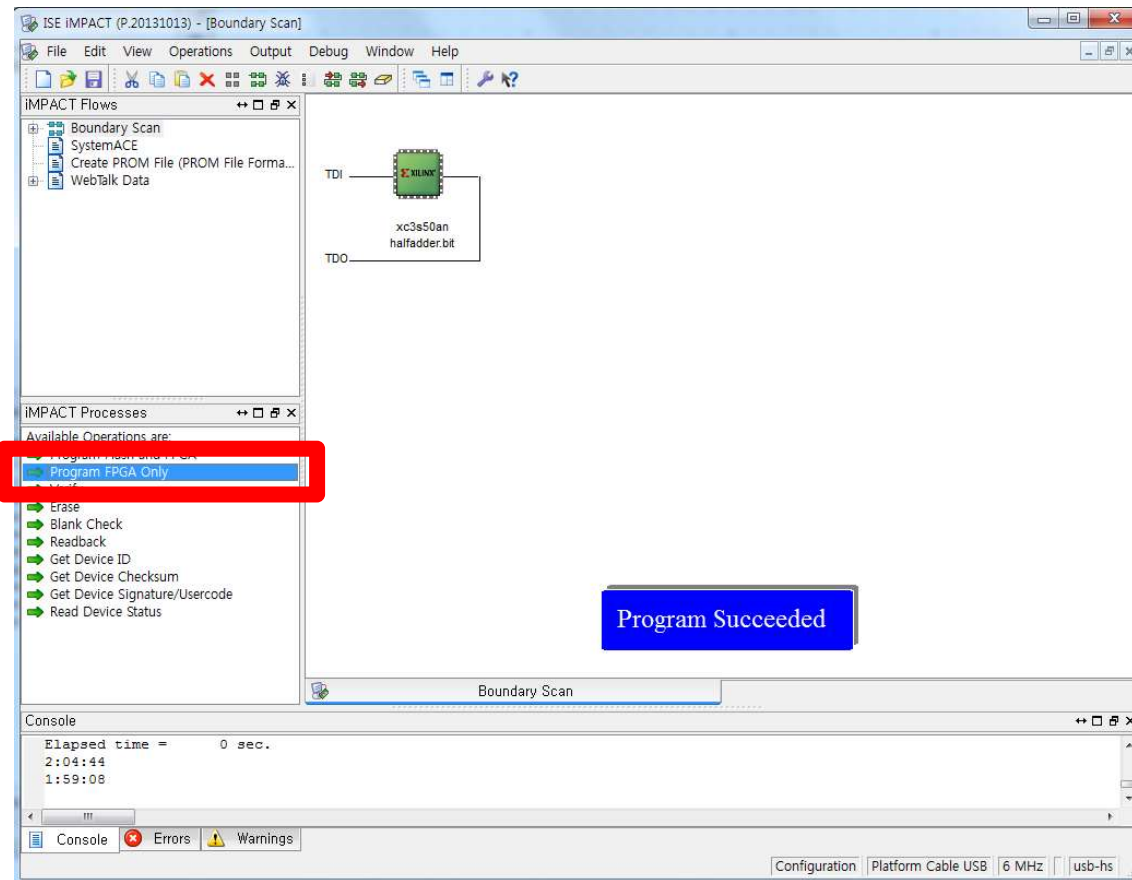

LAB

Vending Machine Structure

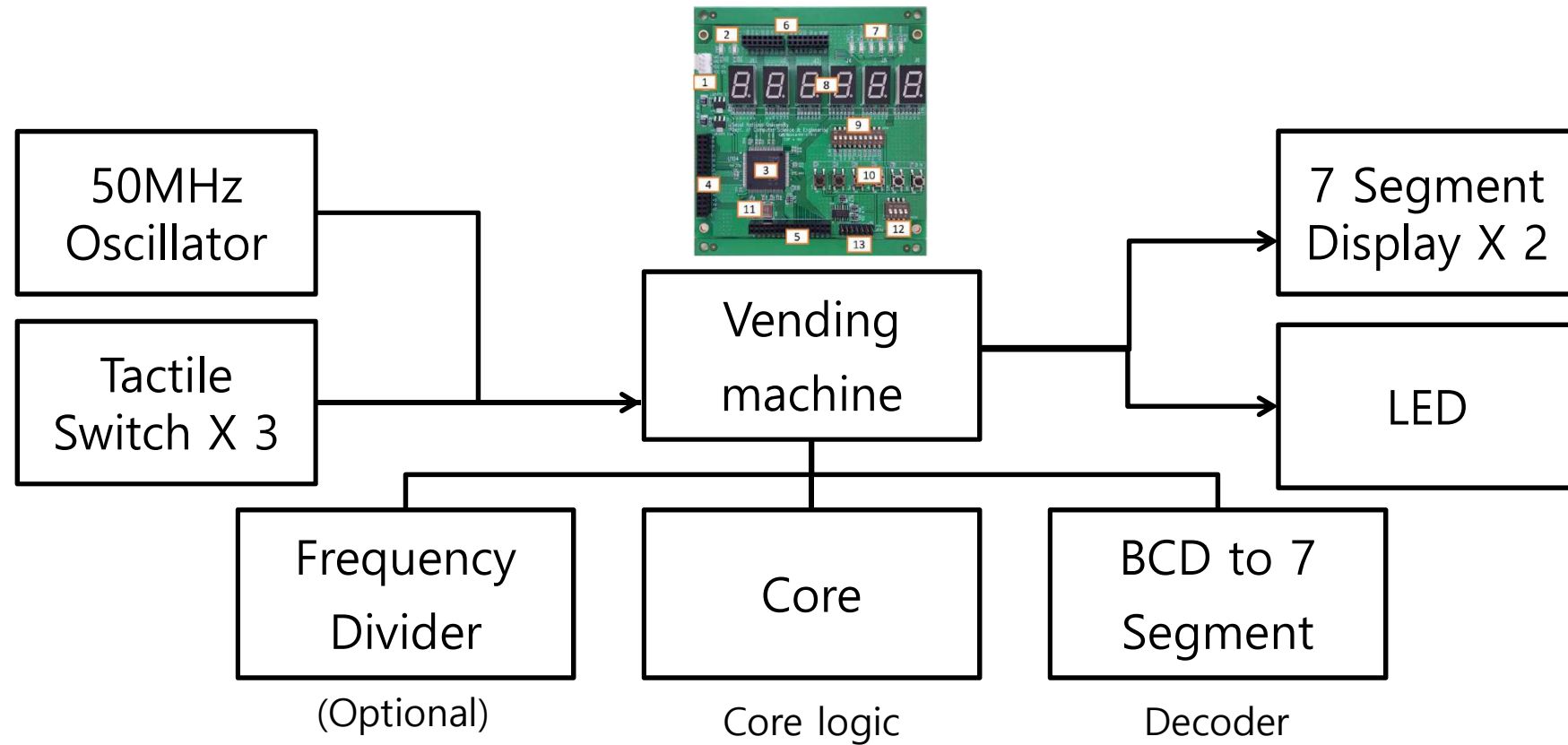

LAB 1

1. Implement **core logic of vending machine** in Verilog. It accept nickels(5 cent) and dimes(10 cent). It has only single coin slot for nickels and dimes. The cost of a drink is 15 cents. It release item without change after 15 cents are deposited. Additionally, your implementation should handle external asynchronous reset signal, it should set the deposit back to 0 when the signal is HIGH. If the deposit is greater than 15 cents, consider it as 15 cents.

LAB 2

2. Implement the **Vending machine** in Verilog and upload your implementation to the Logic Design Board. It accept nickels(5 cent) and dimes(10 cent). It has only single coin slot for nickels and dimes. The cost of a drink is 15 cents. It release item without change after 15 cents are deposited. Additionally, your implementation should handle external asynchronous reset signal, it should set the deposit back to 0 when the signal is HIGH. If the deposit is greater than 15 cents, consider it as 15 cents. Use 50MHz oscillator as clock input, and a tactile switch as reset button and coin inputs. For outputs, use two 7-segment displays as your deposit status, and led as release status.

Report

- **Core logic of vending machine**

- 1. Result of simulation

- All possible case of coin inputs
 - Deposit and release status should be 0 when reset = 1

- **Vending machine**

- 1. All Verilog source code

- should include code for module, submodule (i.e., Vending machine, core logic, BCD-7 seg decoder)
 - only module code, **no test bench code**

- 2. Result of implementation

- Pictures of all possible states that you design

- **Discussion**

(Optional) Study and compare Moore and Mealy machine

Sample Code (Behavioral Description)

```
`timescale 1ns / 1ps

module freq_divider(
    input clr,
    input clk,
    output reg clkout
);
    reg[31:0] cnt;
    always@ (posedge clk) begin
        if(clr) begin
            cnt <= 32'd0;
            clkout <= 1'b0;
        end
        else if (cnt == 32'd25000000) begin
            cnt <= 32'd0;
            clkout <= ~clkout;
        end
        else begin
            cnt <= cnt + 1;
        end
    end
end

endmodule
```


Frequency Divider

```
1 `timescale 1ns / 1ps
2
3 module bcd_to_7(
4     input [3:0] bcd,
5     output reg [6:0] seg
6 );
7
8     always@(bcd) begin
9         case(bcd)
10             4'd0: seg <= 7'b0111111;
11             4'd1: seg <= 7'b0000110;
12             4'd2: seg <= 7'b1011011;
13             4'd3: seg <= 7'b1001111;
14             4'd4: seg <= 7'b1100110;
15             4'd5: seg <= 7'b1101101;
16             4'd6: seg <= 7'b1111101;
17             4'd7: seg <= 7'b0000111;
18             4'd8: seg <= 7'b1111111;
19             4'd9: seg <= 7'b1101111;
20         endcase
21     end
22
23 endmodule
```

BCD to 7-segment Decoder

Homework

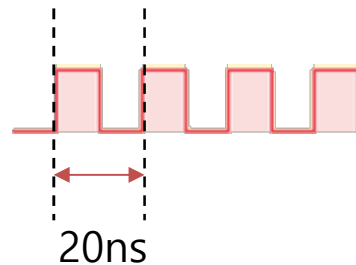- Simulating 50MHz clock in test bench
 - 50MHz : period is 20ns
(So we should flip clock every 10ns)



```
`timescale 1ns / 1ps

module counter_sim;

    // Inputs
    reg clk;
    reg reset;

    // Outputs
    wire [6:0] cnt;

    // Instantiate the Unit Under Test (UUT)
    counter uut (
        .clk(clk),
        .reset(reset),
        .cnt(cnt)
    );

    always #10 clk=~clk;

    initial begin
        // Initialize Inputs
        clk = 0;
        reset = 1;
    end

endmodule
```

Report

- Write a report
 - Either in Korean or in English
 - **Your report should include**
 - Discussion
 - Homework
 - # of pages doesn't matter
 - Documents should be submitted as PDF file(**less than 25Mb**)
 - **Attach source code and waveform screenshot**
 - Due :
 - Class 001 - May, 23th (Before class begin at 7:00pm)
 - Class 002 - May, 24th (Before class begin at 7:00pm)
 - Class 003 - May, 25th (Before class begin at 7:00pm)