

Lab. 03

Logic Design Lab.

Spring 2022

Prof. ChangGun Lee

(cglee@snu.ac.kr)

TA. Hayeon Park

TA. Haejoo Jeon

TA. Seohwan Yoo


(rubis.ld.ta@gmail.com)

Contents

- Multiplexer, Demultiplexer
- Encoder, Decoder
- Verilog
- Lab
 - Implement a Decoder using Verilog
 - Implement a 3-to-8 Decoder using a 2-to-4 Decoder


Multiplexer, Demultiplexer

Multiplexer and Demultiplexer

 

C_1	C_0	M
0	0	X_0
0	1	X_1
1	0	X_2
1	1	X_3

 - 2^n inputs, 1 outputs
- Selection lines exist




C_1	C_0	Selected Output
0	0	$Y_0 = X$ Other outputs 0
0	1	$Y_1 = X$ Other outputs 0
1	0	$Y_2 = X$ Other outputs 0
1	1	$Y_3 = X$ Other outputs 0

- 1 inputs, 2^n outputs
- Selection lines exist


Encoder, Decoder

Encoder, Decoder

 

G	Y0	Y1	Y2	Y3	A	B
1	1	0	0	0	0	0
1	0	1	0	0	0	1
1	0	0	1	0	1	0
1	0	0	0	1	1	1

 - 2^n inputs, n outputs
- Outputs the binary value of the selected input
- No selection lines exist



G	A	B	Y0	Y1	Y2	Y3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

- n inputs, 2^n outputs
- Selects one of 2^n outputs by decoding the binary value on the n inputs
- No selection lines exist


Verilog

Overview


- Hardware description languages (HDLs)
 - We will focus on Verilog
- Verilog Basics
 - Verilog Notations
 - Verilog Operators
 - Verilog Keywords & Constructs
- Types of programming (description)
 - Structural description
 - Data-flow style description
 - Behavioral description

FPGA development process

- FPGA(Field-Programmable Gate Array)

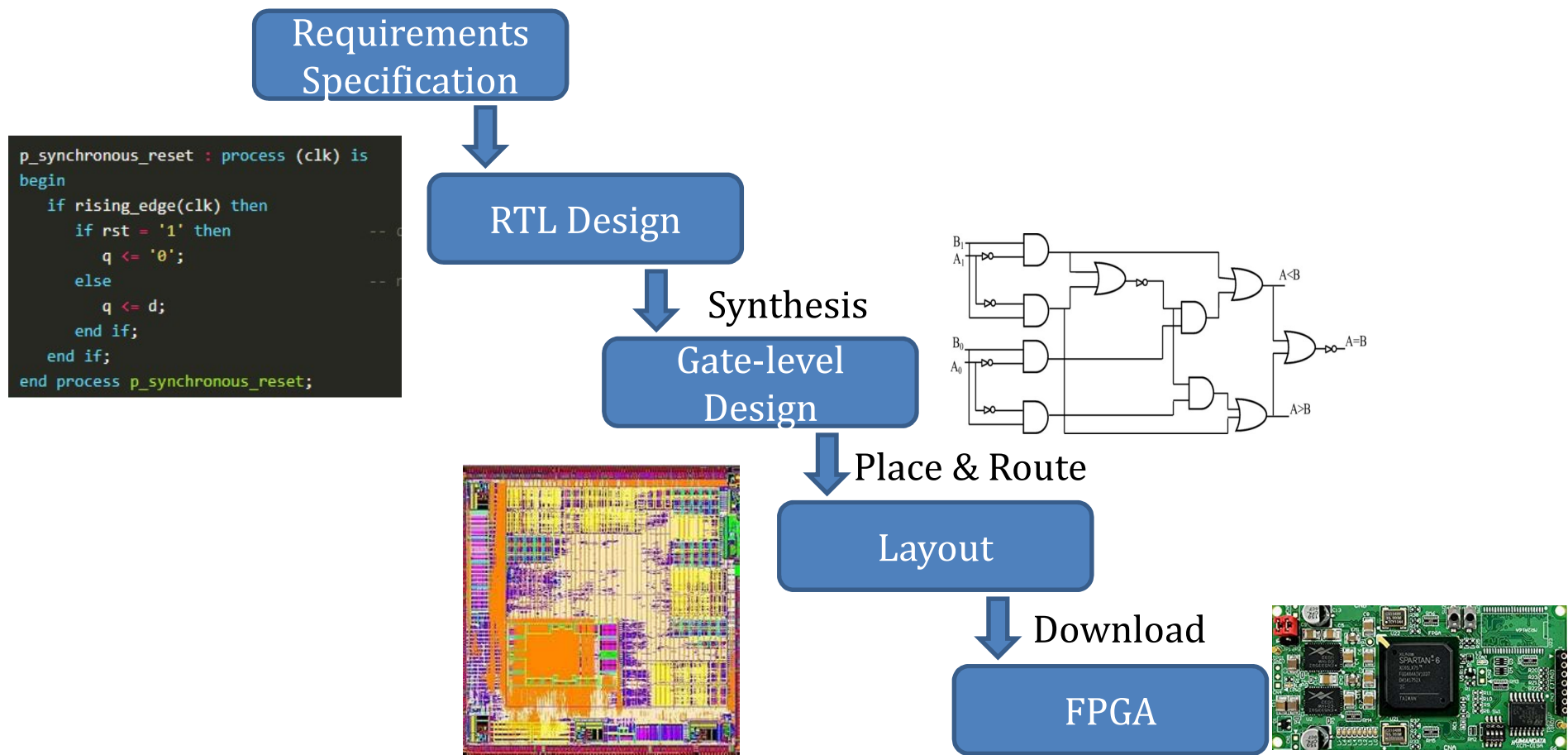

Hardware description languages (HDLs)

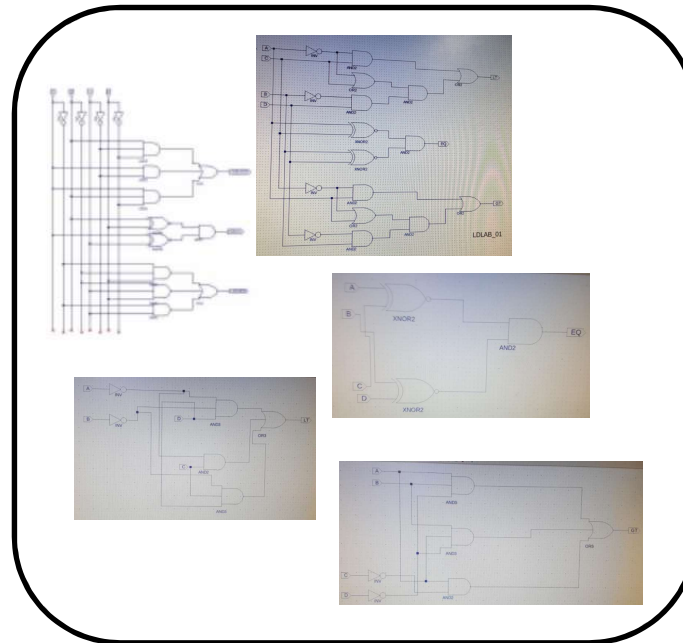

2-bit Comparator

- Hard to understand
- Too many papers...
 - ➔ **Let's make standard HDL !**

Verilog Basics : Verilog Notations (1)

- Verilog is **Hardware Description** Language
- Verilog is:
 - Case sensitive
 - Based on the programming language C
- Comments:
 - `// this is a comment` Single line
 - `/* this is a comment */` Multiple line
- Statement terminator:
 - Every statement should be terminated with ; (semi-colon)

Verilog Basics : Verilog Notations (2)

■ Literals

- **[bit_size]'[base_format][value]**

Example > below literals represent same value

8'b10100001

8'hA1

8'd161

■ Identifiers

- **Scalar (always 1 bit)**

Example > below identifiers are similar with single variable in C

A, B, myA, myB...

- **Vector (bit size is specified as [high_bit:low_bit])**

Example > below identifiers are similar with array variable in C


arrA[7:0], arrB[15:0], arrMyA[7:0], arrMyB[15:0]...

Verilog Basics : Verilog Operators (1)

■ Bitwise Operators

- ~ NOT
- & AND
- | OR
- ^ XOR

Example >

 

```
35 module ex1(  
36     input [3:0] ex_in0,  
37     input [3:0] ex_in1,  
38     output [3:0] ex_out  
39 )  
40  
41     assign ex_out = ex_in0 & ex_in1;  
42  
43 endmodule
```

Verilog Basics : Verilog Operators (2)


- Logical & Relational Operators
 - &&, |, ==, !=, >=, <=, >, <, etc.
- Arithmetic Operators
 - +, -, etc.
- Conditional Operators
 - Condition ? expression1 : expression2;
- Concatenation, Shift, Reduction...

Verilog Basics : Verilog Keywords & Constructs (1)

- Module declaration
 - Start with **module**, end with **endmodule**
- Module IO port declaration
 - Inputs use keyword, **input**, Outputs use keyword **output**.

 Example >

```
21 module ex1(  
22     input ex_in0_scalar,  
23     input ex_in1_scalar,  
24     output ex_out_scalar,  
25     input [3:0] ex_in0_vector,  
26     input [3:0] ex_in1_vector,  
27     output [3:0] ex_out_vector  
28 );  
29  
30 assign ex_out_scalar = ex_in0_scalar & ex_in1_scalar;  
31 assign ex_out_vector = ex_in0_vector & ex_in1_vector;  
32  
33 endmodule
```




Verilog Basics : Verilog Keywords & Constructs (2)

■ Wire Declaration

- Scalar Example : `wire t1, t2;`
- Vector Example : `wire[7:0] t1, t2;`

 Example >

```
21 module ex1(  
22     input A,  
23     input B,  
24     input C,  
25     output Output  
26 );  
27  
28     wire tmp;  
29  
30     assign tmp = A & B;  
31     assign Output = tmp & C;  
32  
33 endmodule
```



Verilog Basics : Verilog Keywords & Constructs (3)

■ Primitive Gates


- not, and, or, nand, nor, xor, xnor

- Syntax:

[gate_operator] [instance_identifier] [(output, input_1, input_2, ...)]

 Example >

```
21 module ex1 (  
22     input A,  
23     input B,  
24     input C,  
25     output Output  
26 );  
27   
28     wire tmp;  
29   
30     and (tmp, A, B);  
31     and (Output, tmp, C);  
32   
33 endmodule
```



Verilog Basics : Verilog Keywords & Constructs (4)

■ Process

- The body of a process consists of procedural statement to make desired outputs from inputs as like a common programming
 - **initial** – executes only once beginning at $t = 0$.
 - **Syntax:**
`initial Statement;`
 - **Example >**
`initial begin`
`Statement;`
`Statement;`
`...`
`end`
 - **always** – executes at $t = 0$ and repeatedly thereafter following repeat conditions.
 - **Syntax:**
`always Repeat condition`
`Statement;`
 - **Example >**
`always Repeat condition begin`
`Statement;`
`Statement;`
`...`
`end`

Verilog Basics : Verilog Keywords & Constructs (5)

- Timing Control Statement (for repeat conditions)

Type	Syntax	Description
Delay Control	#10	Delay 10 unit time
Event Control	@(a)	Wait until signal 'a' is changed
	@(posedge a) @(negedge a)	Wait until signal 'a' is changed to '1' Wait until signal 'a' is changed to '0'
Level Control	wait (a==0)	Wait until signal 'a' is equal to '0'

- The body of the process consists of procedural assignments
 - Blocking assignments
 - Example: $C = A + B$;
 - Execute sequentially as in a programming language
 - Non-blocking assignments
 - Example: $C <= A + B$;
 - Evaluate right-hand sides, but do not make any assignment until all right-hand sides evaluated. Execute concurrently unless delays are specified.

Verilog Basics : Verilog Keywords & Constructs (6)

Examples > blocking vs. Non-blocking

```
Always @(*)  
begin  
  B = A;  
  C = B;  
end
```

- Suppose initially A = 0, B = 1, and C = 2. After execution, B = 0 and C = 0.

```
Always @(*)  
begin  
  B <= A;  
  C <= B;  
end
```

- Suppose initially A = 0, B = 1, and C = 2. After execution, B = 0 and C = 1.

Verilog Basics : Verilog Keywords & Constructs (7)

- Because of the use of procedural rather than continuous assignment statements, assigned values must be retained over time.
 - Register type: `reg`
 - The `reg` in contrast to `wire` stores values between executions of the process
 - A `reg` type does not imply hardware storage!

Verilog Basics : Verilog Keywords & Constructs (8)

■ Conditional constructs


- The **if-else**
 if (*condition*)
 begin *procedural statements* **end**
 {**else if** (*condition*)
 begin *procedural statements* **end**}
 else
 begin *procedural statements* **end**
- The **case**
 case expression
 {**case** expression : statements}
 endcase;

Types of programming (description)

- Describe hardware at varying levels of abstraction
 - **Structural description**
 - Textual replacement for schematic
 - **Data-flow style description**
 - Textual replacement of truth table
 - **Behavioral/functional description**
 - Define just WHEN, WHAT, not HOW

Tutorials

1. Design Structure

 

New Source Wizard

Define Module
Specify ports for module.


Module name: v74x139h

Port Name	Direction	Bus	MSB	LSB
G	input	<input type="checkbox"/>		
A	input	<input type="checkbox"/>		
B	input	<input type="checkbox"/>		
Y	output	<input checked="" type="checkbox"/>	3	0
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		

More Info < Back Next > Cancel

```
3 module v74x139h(  
4     input G,  
5     input A,  
6     input B,  
7     output [3:0] Y  
8 );  
9  
10  
11 endmodule
```

2-1. Structural Description

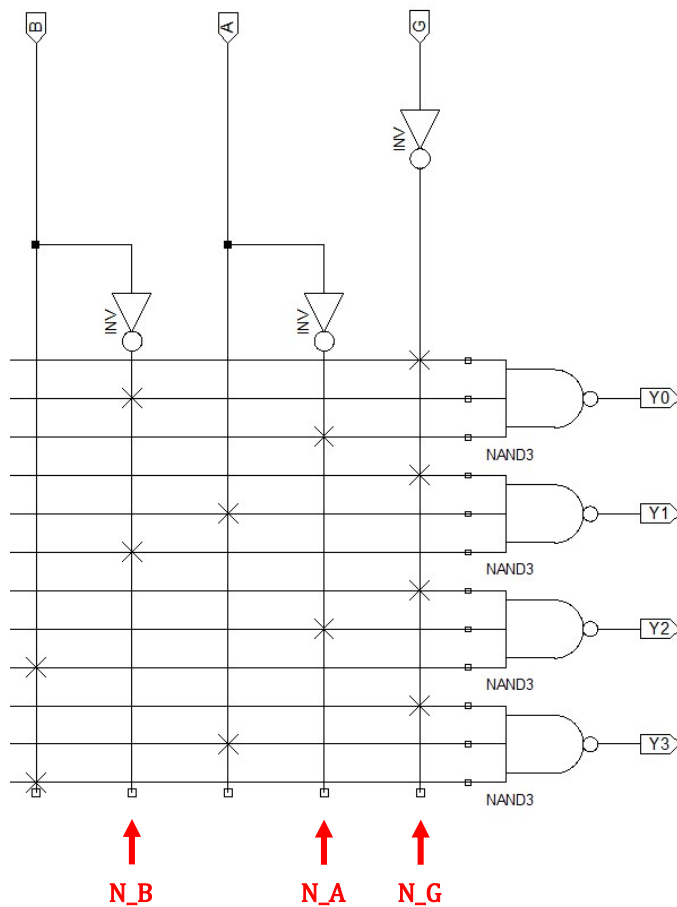

```
3 module v74x139h(  
4     input G,  
5     input A,  
6     input B,  
7     output [3:0] Y  
8 );  
9  
10 wire N_A, N_B, N_G;  
11  
12 not T1(N_G, G);  
13 not T2(N_A, A);  
14 not T3(N_B, B);  
15  
16 nand T4(Y[0], N_G, N_A, N_B);  
17 nand T5(Y[1], N_G, A, N_B);  
18 nand T6(Y[2], N_G, N_A, B);  
19 nand T7(Y[3], N_G, A, B);  
20  
21 endmodule
```

Textual representation of schematic

2-2. Data Flow Description

B	A	G	Y[3:0]
0	0	0	1110
0	1	0	1101
1	0	0	1011
1	1	0	0111
0	0	1	1111
0	1	1	1111
1	0	1	1111
1	1	1	1111


```
3 module v74x139h(  
4     input G,  
5     input A,  
6     input B,  
7     output [3:0] Y  
8 );  
9  
10 wire [1:0] sel;  
11 wire [3:0] out;  
12  
13 assign sel = {B, A};  
14 assign Y = ~out;  
15  
16 assign out = (sel == 2'b00 && G == 1'b0) ? 4'b0001 :  
17             (sel == 2'b01 && G == 1'b0) ? 4'b0010 :  
18             (sel == 2'b10 && G == 1'b0) ? 4'b0100 :  
19             (sel == 2'b11 && G == 1'b0) ? 4'b1000 :  
20             4'b0000;  
21  
22 endmodule
```

Textual representation of truth table

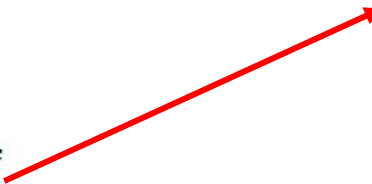2-3. Behavioral Description

```
3 module v74x139h(  
4     input G,  
5     input A,  
6     input B,  
7     output [3:0] Y  
8 );  
9  
10    wire [1:0] sel;  
11    reg [3:0] out;  
12  
13    assign sel = {B, A};  
14    assign Y = ~out;  
15  
16    always@(G or sel) When?  
17    begin  
18        if (G == 1'b0)  
19        begin  
20            case(sel)  
21                2'b00 : out = 4'b0001;  
22                2'b01 : out = 4'b0010;  
23                2'b10 : out = 4'b0100;  
24                2'b11 : out = 4'b1000;  
25            endcase  
26        end  
27  
28  
29  
30  
31    end  
32  
33 endmodule
```

If there is no else-block,
reg out will be synthesized as storage



Which action?

2-4. Unify Modules

```
3 module v74x139(  
4     input G1,  
5     input G2,  
6     input B1,  
7     input B2,  
8     input A1,  
9     input A2,  
10    output [3:0] Y1,  
11    output [3:0] Y2  
12 );  
13  
14    v74x139h T1(.G(G1), .A(A1), .B(B1), .Y(Y1));  
15    v74x139h T2(.G(G2), .A(A2), .B(B2), .Y(Y2));  
16  
17 endmodule
```

It is same as using gate primitives


Lab

Today


1. Design a 74x139 using Verilog.

- 1) Practice all the designing methods for half 74x139 each and simulate them
- 2) Implement a 74x139 and simulate it

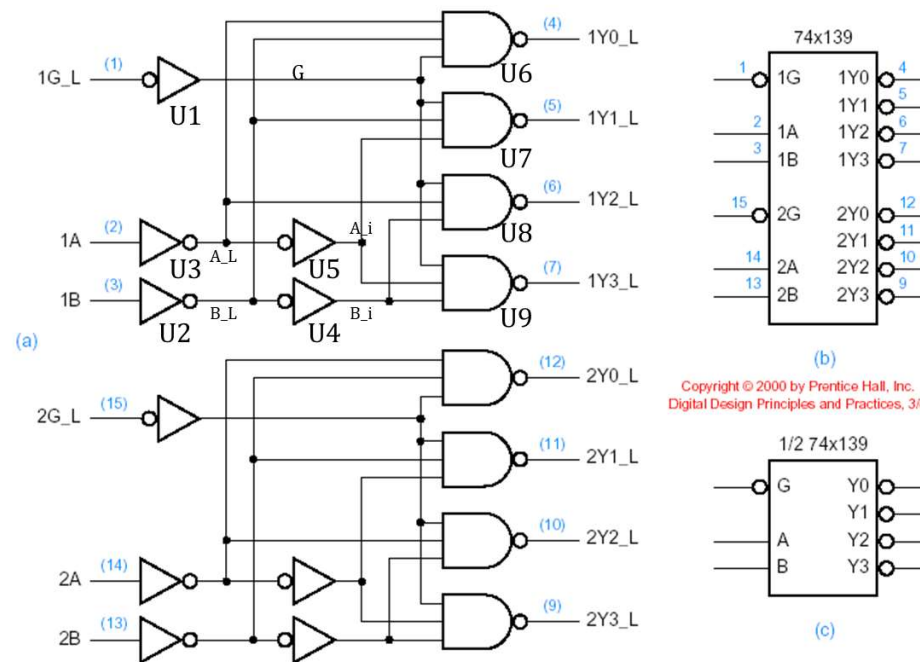
2. Design a 3-to-8 decoder using 2-to-4 decoders only and simulate it. (one of 3 designing methods)



Create a new Verilog project

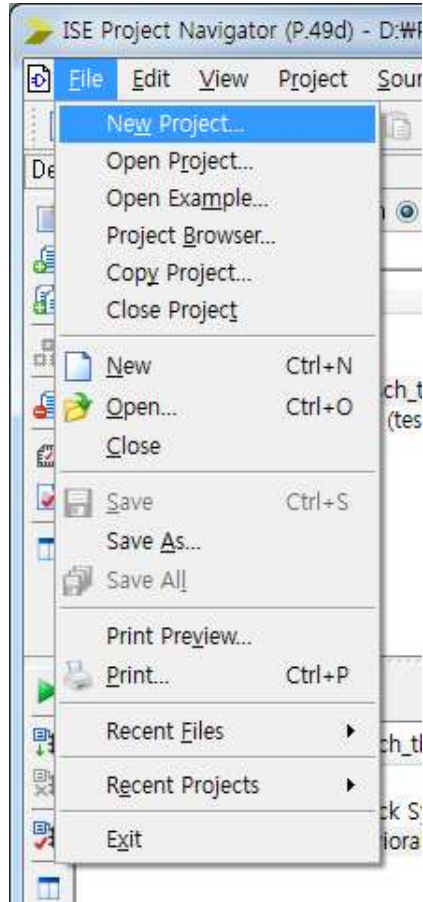

Set the project name, location, type

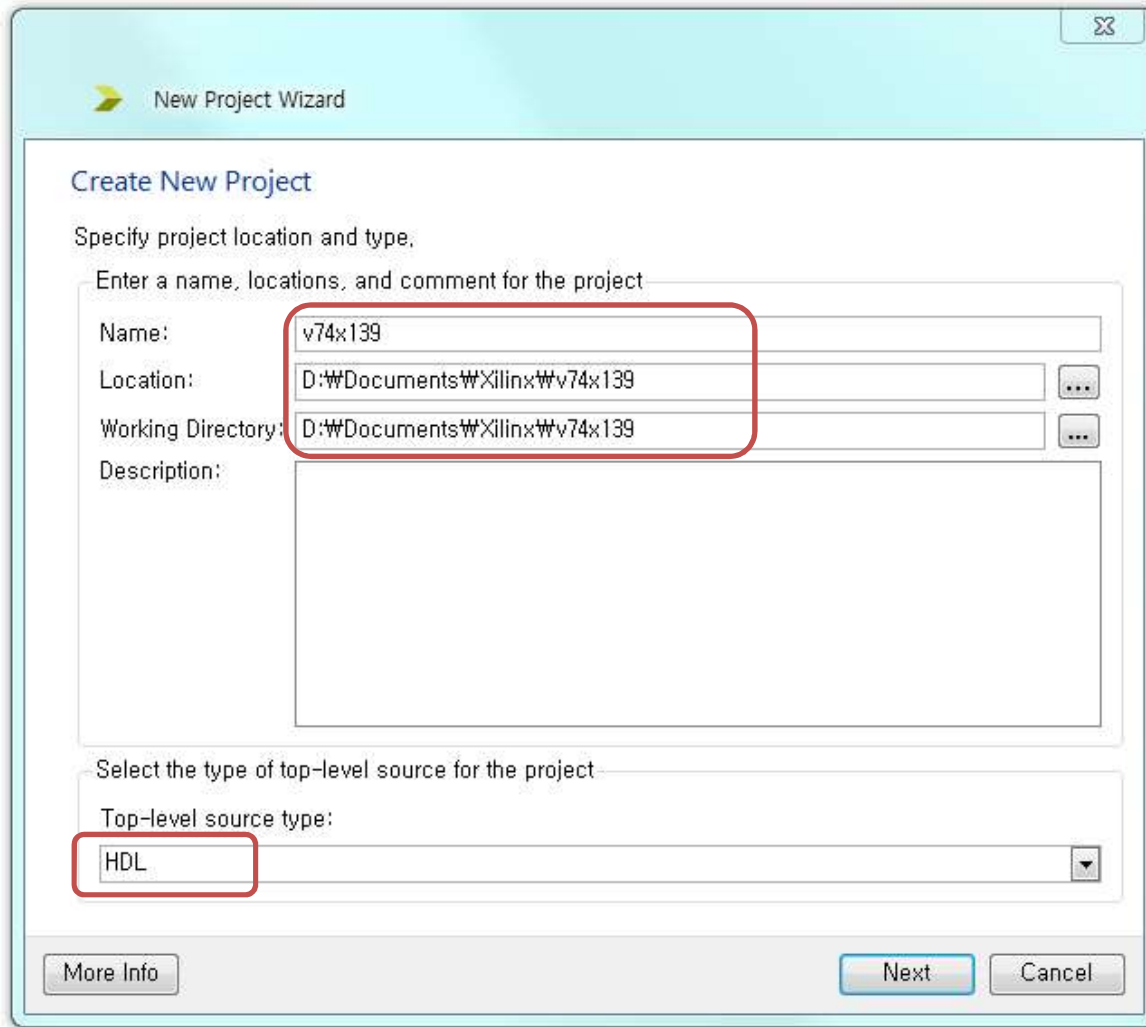

The image shows a 'New Project Wizard' dialog box with a light blue header. The main area is titled 'Create New Project' and contains instructions to 'Specify project location and type' and 'Enter a name, locations, and comment for the project'. There are four input fields: 'Name:', 'Location:', 'Working Directory:', and 'Description:'. The 'Name', 'Location', and 'Working Directory' fields are grouped by a red rectangle and contain the text 'v74x139', 'D:\Documents\Xilinx\v74x139', and 'D:\Documents\Xilinx\v74x139' respectively. The 'Description' field is empty. Below these fields is a section titled 'Select the type of top-level source for the project' with a dropdown menu labeled 'Top-level source type:' showing 'HDL'. At the bottom, there are three buttons: 'More Info', 'Next', and 'Cancel'.

New Project Wizard

Create New Project

Specify project location and type.

Enter a name, locations, and comment for the project

Name: v74x139

Location: D:\Documents\Xilinx\v74x139

Working Directory: D:\Documents\Xilinx\v74x139


Description:

Select the type of top-level source for the project

Top-level source type: HDL

More Info Next Cancel


Set the project name, location, type

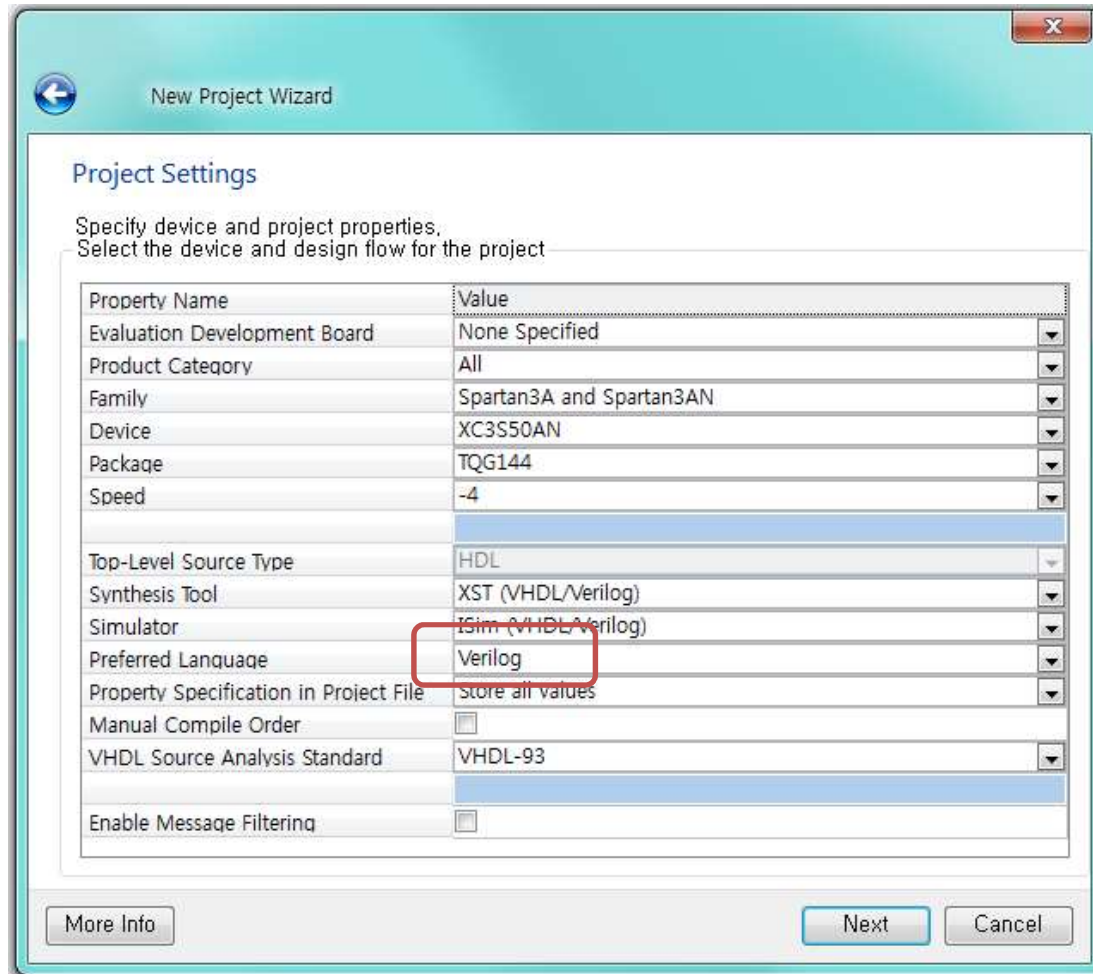

The image shows a 'New Project Wizard' dialog box with a 'Project Settings' tab. The dialog has a title bar with a back arrow, the text 'New Project Wizard', and a close button. Below the title bar, the 'Project Settings' section is titled 'Specify device and project properties. Select the device and design flow for the project'. It contains a table of properties with dropdown menus for most values. A red rectangle highlights the 'Preferred Language' property, which is set to 'Verilog'. At the bottom of the dialog are three buttons: 'More Info', 'Next', and 'Cancel'.

Property Name	Value
Evaluation Development Board	None Specified
Product Category	All
Family	Spartan3A and Spartan3AN
Device	XC3S50AN
Package	TQG144
Speed	-4
Top-Level Source Type	HDL
Synthesis Tool	XST (VHDL/Verilog)
Simulator	ISim (VHDL/Verilog)
Preferred Language	Verilog
Property Specification in Project File	Store all values
Manual Compile Order	<input type="checkbox"/>
VHDL Source Analysis Standard	VHDL-93
Enable Message Filtering	<input type="checkbox"/>

Create a new Verilog source

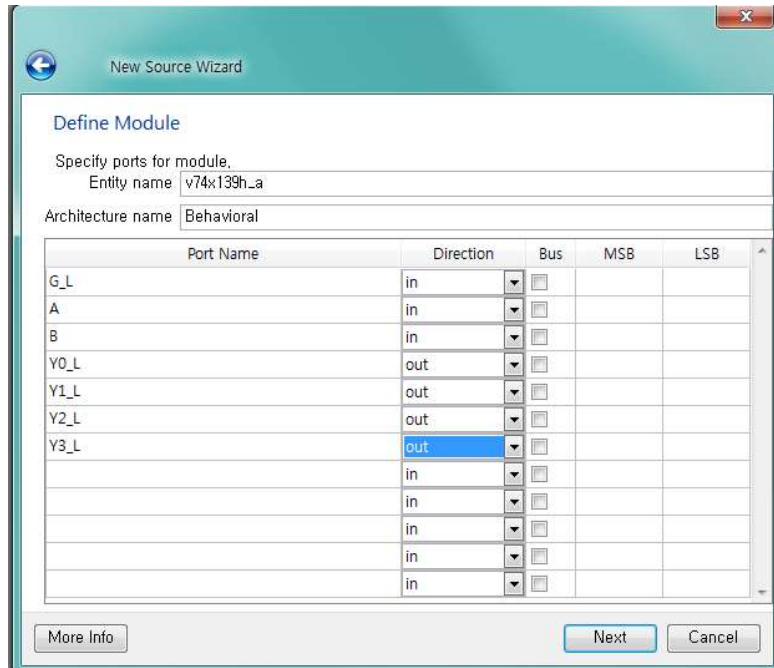

New Source Wizard

Define Module

Specify ports for module.


Entity name: v74x139h_a

Architecture name: Behavioral

Port Name	Direction	Bus	MSB	LSB
G_L	in	<input type="checkbox"/>		
A	in	<input type="checkbox"/>		
B	in	<input type="checkbox"/>		
Y0_L	out	<input type="checkbox"/>		
Y1_L	out	<input type="checkbox"/>		
Y2_L	out	<input type="checkbox"/>		
Y3_L	out	<input type="checkbox"/>		
	in	<input type="checkbox"/>		
	in	<input type="checkbox"/>		
	in	<input type="checkbox"/>		
	in	<input type="checkbox"/>		
	in	<input type="checkbox"/>		

More Info Next Cancel

or

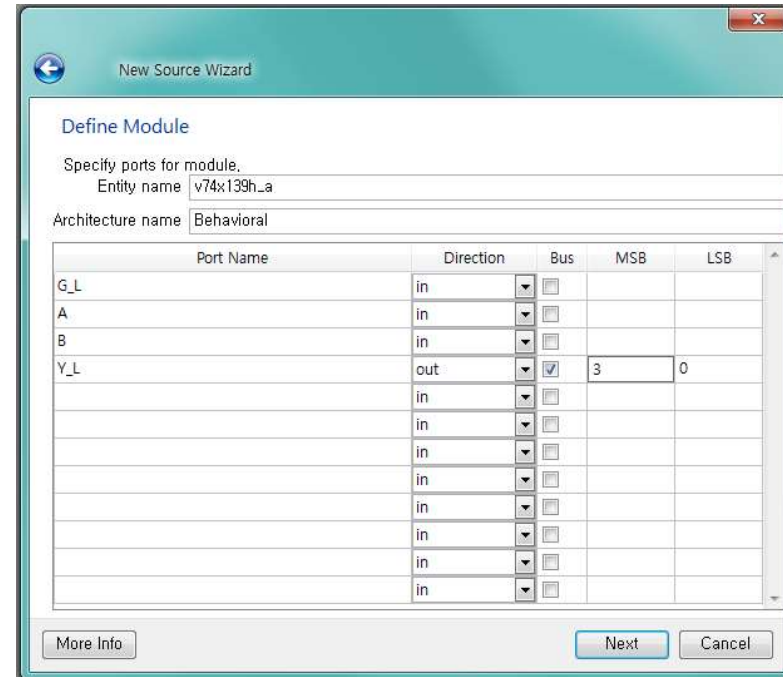

New Source Wizard

Define Module

Specify ports for module.

Entity name: v74x139h_a

Architecture name: Behavioral


Port Name	Direction	Bus	MSB	LSB
G_L	in	<input type="checkbox"/>		
A	in	<input type="checkbox"/>		
B	in	<input type="checkbox"/>		
Y_L	out	<input checked="" type="checkbox"/>	3	0
	in	<input type="checkbox"/>		
	in	<input type="checkbox"/>		
	in	<input type="checkbox"/>		
	in	<input type="checkbox"/>		
	in	<input type="checkbox"/>		
	in	<input type="checkbox"/>		

More Info Next Cancel


Write your own Verilog codes

```
3 module v74x139h(  
4     input G,  
5     input A,  
6     input B,  
7     output [3:0] Y  
8 );  
9  
10    wire N_A, N_B, N_G;  
11  
12    not T1(N_G, G);  
13    not T2(N_A, A);  
14    not T3(N_B, B);  
15  
16    nand T4(Y[0], N_G, N_A, N_B);  
17    nand T5(Y[1], N_G, A, N_B);  
18    nand T6(Y[2], N_G, N_A, B);  
19    nand T7(Y[3], N_G, A, B);  
20  
21 endmodule
```

Compile and check errors

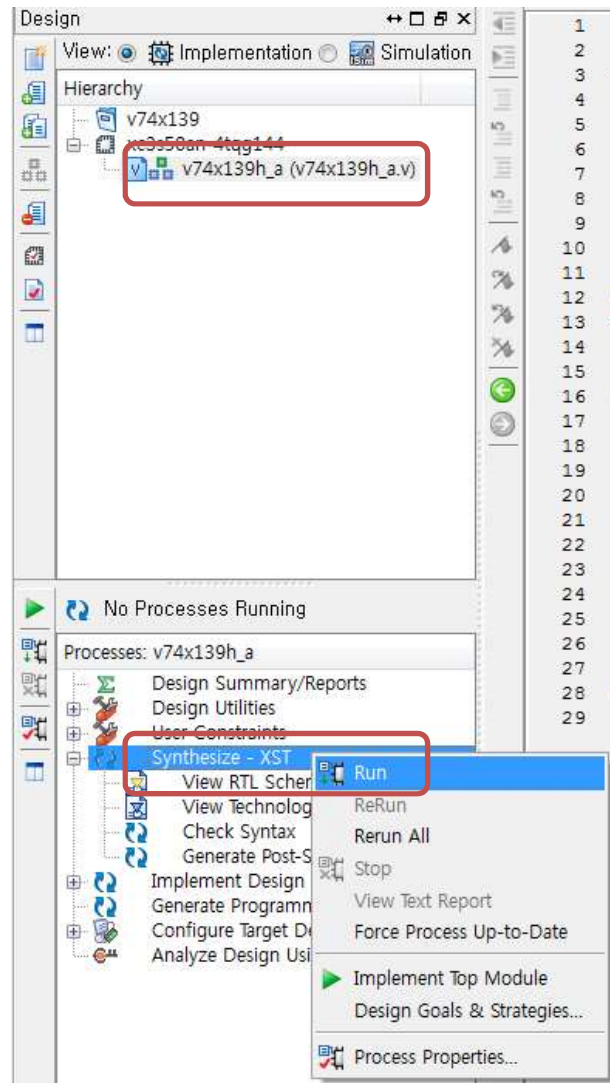

Create a Verilog test bench

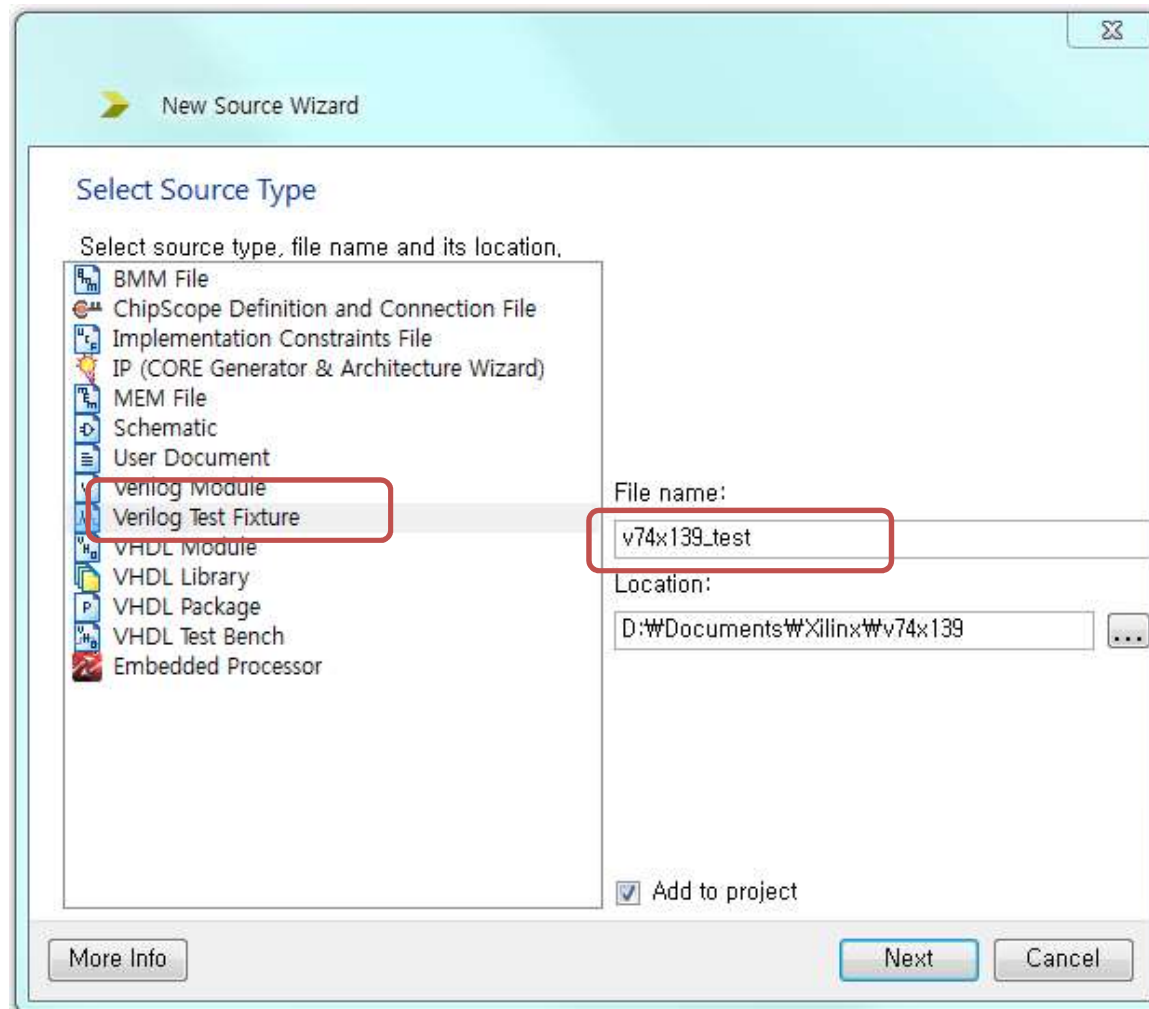

Write a Verilog test bench codes

```
module v74x139h_test;

    // Inputs
    reg G_L;
    reg A;
    reg B;

    // Outputs
    wire Y0_L;
    wire Y1_L;
    wire Y2_L;
    wire Y3_L;

    // Instantiate the Unit Under Test (UUT)
    v74x139h a uut (
        .G_L(G_L),
        .A(A),
        .B(B),
        .Y0_L(Y0_L),
        .Y1_L(Y1_L),
        .Y2_L(Y2_L),
        .Y3_L(Y3_L)
    );

    initial begin
        // Initialize Inputs
        G_L = 0;
        A = 0;
        B = 0;

        // Wait 100 ns for global reset to finish
        #100;


        // Add stimulus here
        G_L = 0;
        A = 1;
        B = 0;

        #100 G_L = 0; A = 0; B = 1;


        #100 G_L = 0; A = 1; B = 1;

        #100;
    end
endmodule
```


Simulate it

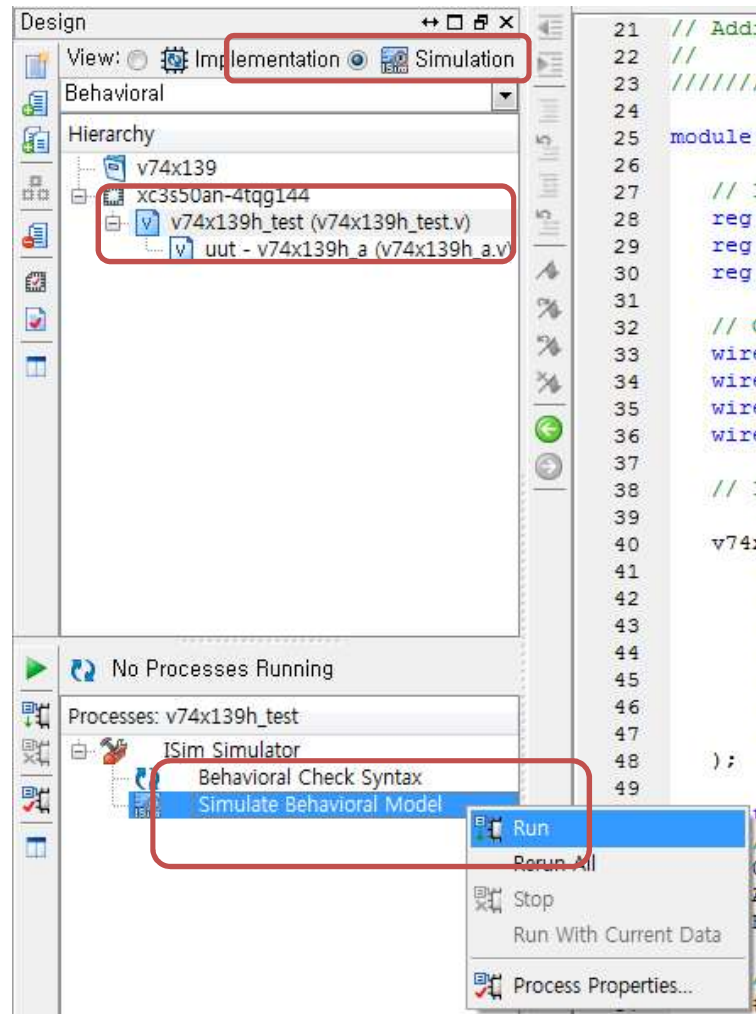

Simulation result

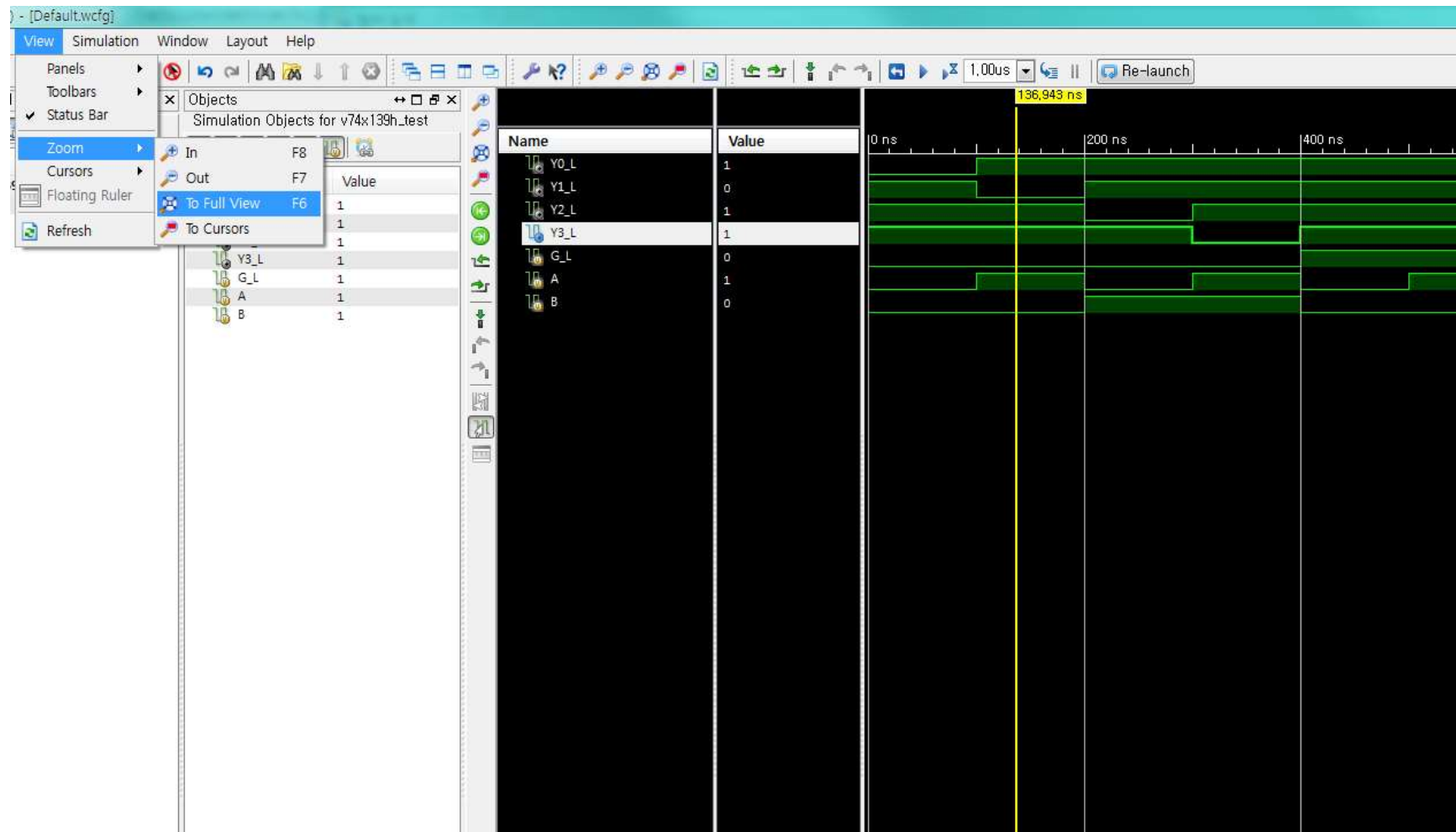

Homework

Homework

(1) Lab Practice

- Implement 74x139 with 3 method and simulate it
- Implement a 3-to-8 decoder using 2-to-4 decoders only and simulate it (one of 3 designing methods)

(2) Implement 4-to-1 MUX with all the designing methods that we practiced and Simulate it.

(3) Discuss about each type of descriptions. (Pros & Cons, etc.)

(Optional) study part of the Verilog grammar and discuss about why it was designed that way

Ex) for loop, while loop, blocking, non-blocking assignments, module based feature, etc.

Report

- Write a report
 - Either in Korean or in English
 - **Your report should include**
 - discussion
 - Homework (if there is any)
 - # of pages doesn't matter
 - Documents should be submitted as **PDF file(less than 25Mb)**
 - **Attach source code and waveform screenshot**
 - Due :
 - Class 001 - April, 11th (Before class begin at 7:00pm)
 - Class 002 - April, 12th (Before class begin at 7:00pm)
 - Class 003 - April, 13th (Before class begin at 7:00pm)